

Permeability :- Magnetic Circuit

The phenomenon of magnetism or electromagnetism are dependant upon certain property of a medium that is called permeability.

$$\text{Absolute permeability } (\mu_0) = 4\pi \times 10^{-7}$$

$$\text{Relative permeability } (\mu_r) = 1$$

Law of Magnetic Force :-

The force between two magnetic poles is directly proportional to their pole strength, inversely proportional to the square of distance between them and inversely proportional to the absolute permeability of the medium.

$$F \propto \frac{m_1 m_2}{\mu r^2}$$

$$\Rightarrow F = K \frac{m_1 m_2}{\mu r^2} N$$

$$\Rightarrow F' = K \frac{m_1 m_2}{\mu r^2} r'$$

$$\Rightarrow F = \frac{K m_1 m_2}{4\pi \epsilon_0 r^2} \times \gamma$$

$$\Rightarrow F = \frac{K m_1 m_2}{4\pi \epsilon_0 r^3} \gamma$$

$$\Rightarrow F = \frac{K m_1 m_2}{4\pi \epsilon_0 r^3} \frac{\gamma}{N}$$

$$\Rightarrow F = \left[\frac{1}{4\pi} \frac{m_1 m_2}{\epsilon_0 r^2} \right] \frac{\gamma}{N}$$

Magnetic field strength (H) :-

Magnetic field strength at any point within a magnetic field is numerically equals to the force experienced by 'N' pole of 1 wb placed at that point.

$$F = K \frac{I \cdot M}{4\pi r^2}$$

$$\Rightarrow H = \frac{K M}{4\pi r^2} \frac{N}{wb}$$

$$\Rightarrow H = \frac{1}{4\pi} \frac{M}{r e \delta^2} \text{ N/wb}$$

Magnetic potential :-

The magnetic potential at any point within a magnetic field is measured by the work done in setting a pole of 1 wb from infinite to that point against the force of magnetic field.

$$M = \frac{K m}{r e \delta}$$

$$\Rightarrow M = \frac{m}{4\pi r e \delta} \text{ J/wb}$$

Flux per unit pole :-

Suppose a unit pole radiates a flux of 1 wb

then it is denoted as ϕ . If the pole radiates a flux of M wb.

$$\text{so } \phi = M \text{ wb.}$$

Flux density :- (B)

It is given that the flux passing per unit area through a plane right angle to it.

$$B = \frac{\phi}{A} \quad \frac{wb}{m^2}$$


Absolute permeability (μ_0) and relative permeability (μ_r): -

The above figure shows a bar magnetic material or a iron piece placed in uniform magnetic field strength of 'H' with flux density 'B'.

Well 'H' is present in the vacuum.

$$B_0 = \mu_0 H$$

Well the iron piece is magnetised by

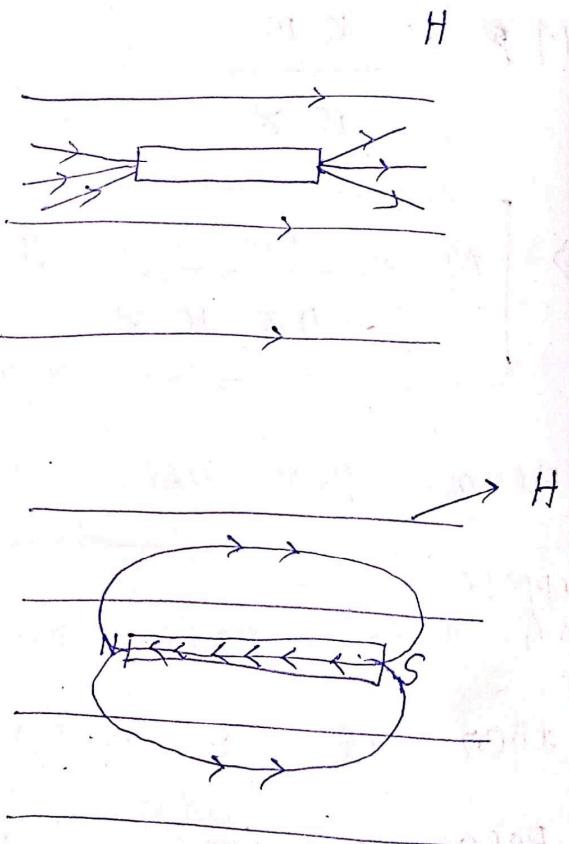

induction, the magnetic flux density

$$B_i = \frac{m}{A}$$

So total,

$$B = B_0 + B_i$$

$$\Rightarrow B = \mu_0 H + \frac{m}{A}$$

$$B = \mu H -$$

$$\Rightarrow B = \mu_0 \mu_s H$$

$$\Rightarrow B = (\mu_0 H) \mu_s$$

$$\Rightarrow B = B_0 \mu_s$$

$$\Rightarrow \mu_s = \frac{B \text{ (medium / material)}}{B_0 \text{ (vacuum)}}$$

Intensity of Magnetisation (I) :-

It is defined as the induced pole strength developed per unit area.

m = pole strength induced in a magnet
in weber.

A = pole area in mm^2

$$I = \frac{m}{A} \quad \frac{\text{wb}}{\text{m}^2}$$

Susceptibility (K) :-

Susceptibility is defined as the ratio of intensity of magnetisation (I) to magnetic force (H).

$$K = \frac{I}{H} \quad \frac{\text{Henry}}{\text{meter}}$$

Relation Between B, H, I, K :-

$$B = \mu H = \mu_0 H + \frac{m}{A}$$

$$\Rightarrow B = \mu_0 H + I$$

$$\mu = \frac{B}{H}$$

$$= \frac{\mu_0 H + I}{H}$$

$$= \mu_0 + \frac{I}{H}$$

$$\Rightarrow \mu = \mu_0 + K$$

$$B = \mu H$$

$$= (\mu_0 + K) H$$

$$= \mu_0 H + K H$$

$$\Rightarrow B = B_0 + K H$$

$$B = \mu H$$

$$\mu = \mu_0 \mu_s$$

$$\mu = \mu_0 + K$$

$$\Rightarrow \mu_0 \mu_s = \mu_0 + K$$

$$\Rightarrow \mu_s = \frac{\mu_0 + K}{\mu_0}$$

$$\Rightarrow \mu_s = 1 + \frac{K}{\mu_0}$$

Consider a solenoid having magnetic path of 'l' meter, area of cross section ' $A \text{ m}^2$ ' and a coil of 'N' turns.

carrying a current of 'I' Amp, then
the magnetic field strength is

$$H = \frac{NI}{l} \text{ A/Wb}$$

$$B = \mu H$$

$$\Rightarrow B = \frac{\mu NI}{l}$$

$$\phi = \text{flux}$$

$$\Rightarrow \phi = BA$$

$$\Rightarrow \phi = \frac{\mu NI A}{l}$$

$$\Rightarrow \phi = \frac{\mu_0 \mu_s N I A}{l}$$

$$\Rightarrow \phi = \frac{\frac{NI}{l}}{\mu_0 \mu_s A} \text{ wb}$$

$\frac{l}{\mu_0 \mu_s A}$ is called reluctance (s)

'NI' is magneto motive force (mmf).

$$\phi = \frac{mmf}{\text{Reluctance}}$$

Reluctance

Magneto motive Force :

- It drives or tends to drive flux through a magnetic circuit like electromotive force (emf) in the electric circuit.
- mmf is equal to the work done in Joules in carrying a unit magnetic pole once through the entire magnetic circuit.
- It measured in Amperes-turn.

Amperes - turn (AT) :

- It is the unit of magnetomotive force (mmf) and is given by the product of number of turns in a magnetic ckt and the current in Ampere in those turns.

Reluctance :- (s)

It is the property of a material which opposes the creation of flux or it opposes the flow of magnetic flux through a material.

$$S = \frac{l}{Re \cdot A} = \frac{l}{Re \operatorname{res} A}$$

$$\text{unit} = \frac{1}{\text{Henzry}}$$



Permeance :-

It is the reciprocal of reluctance or readiness for flow of magnetic flux.

Reluctivity :-

It is the specific Reluctance.



parallel magnetic circuit :-

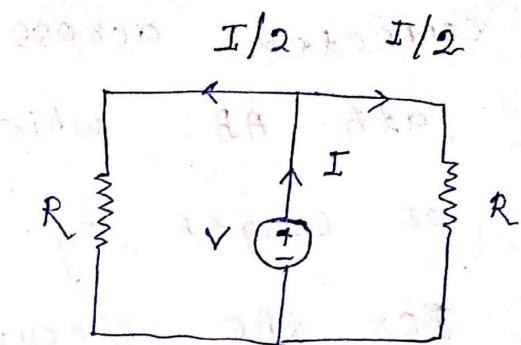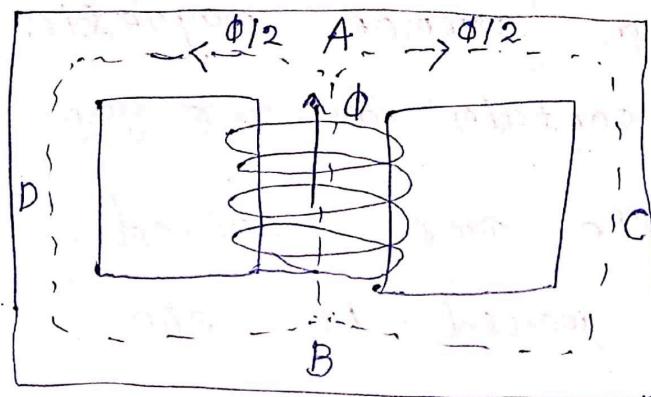

The above figure shows a parallel magnetic circuit consisting of two parallel magnetic path ACB and ADB given by same mmf.


The flux produced by the coil wound on a central core is divide equally at point 'A' between two outer parallel path.

Series parallel magnetic circuit :-

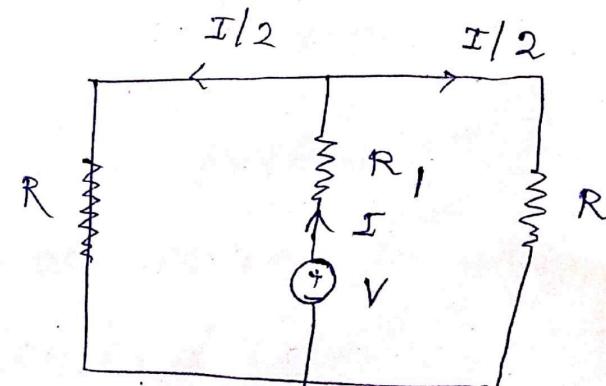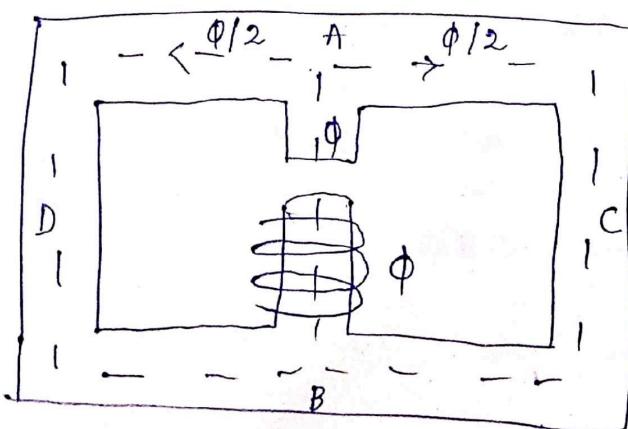


The above figure shows two parallel magnetic circuit ACB and ADB connected across a common magnetic path AB which contains an air gap of length l_g . The mmf required for the circuit would be the sum of,

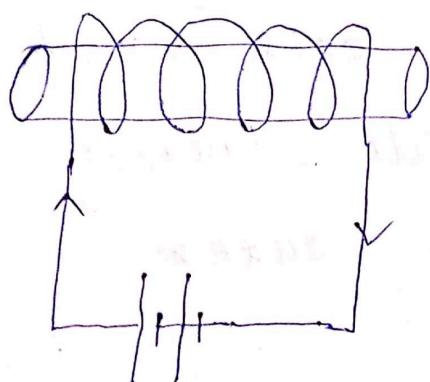- (i) that required for the air gap.
- (ii) that required for the parallel circuit.



B - H curve :-

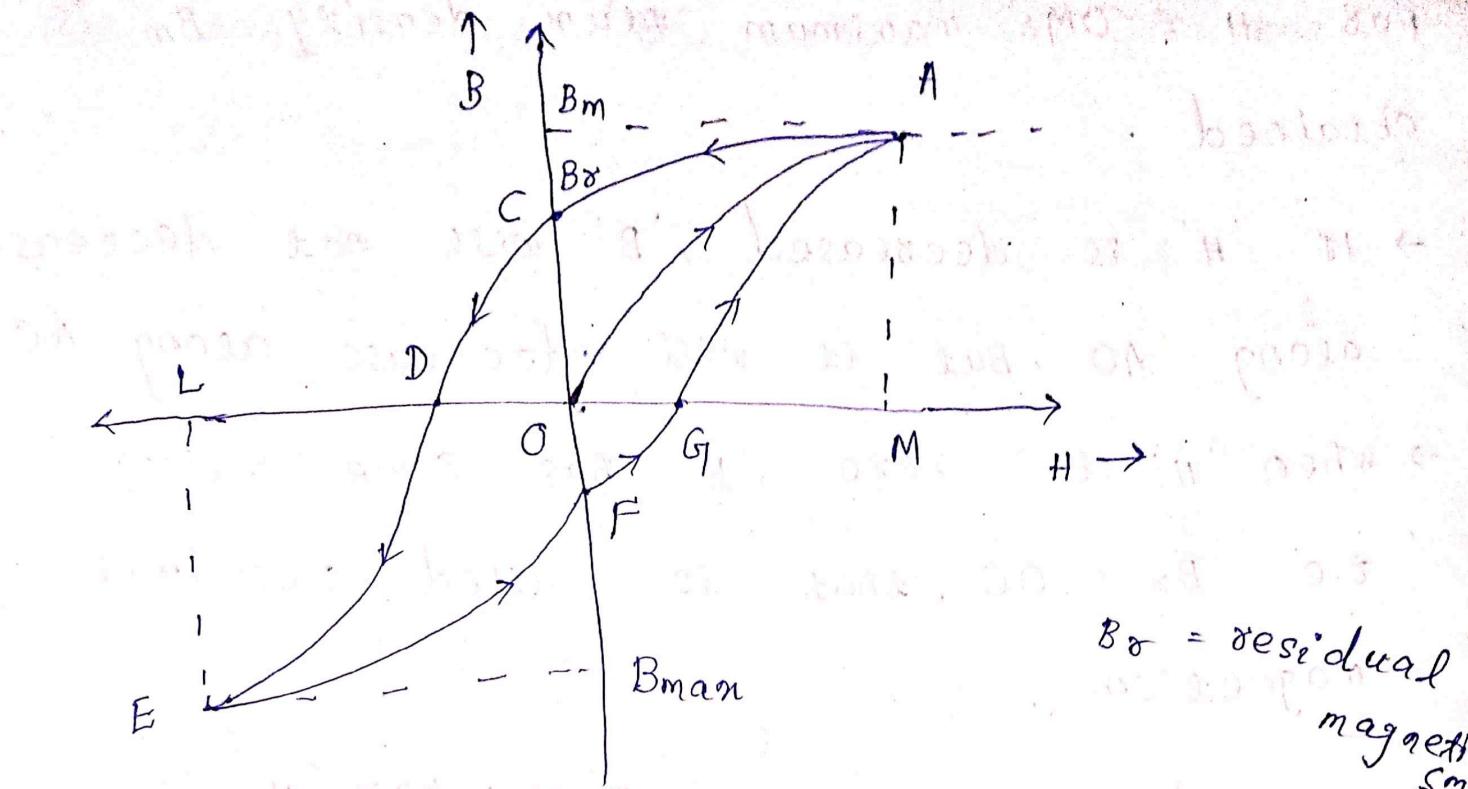

B_r = residual magnetism

→ It is defined as the lagging of magnetic flux density 'B' behind the magnetising force 'H'

Let us take an unmagnetised iron piece AB and magnetise it by placing within a field of solenoid. Then,

$$H = \frac{NI}{l}$$

Let 'H' is increase from '0' to a maximum value then corresponding B value is noted.

If we plot the relation between H and B a curve like OA as shown in the above figure is obtained.



For $H = 0$ M maximum flux density B_m is obtained.

- If ' H ' is decreased, ' B ' will not decrease along AO. But it will decrease along AC.
- When ' H ' is zero, ' B ' has some value i.e. $B_x = OC$, that is called residual magnetism.
- To demagnetise the iron bar ' H ' is reversed. Then ' B ' is reduced to zero at point 'D'. where $H = OD$ and $B = 0$.
- Again when ' H ' value is further increased in -ve direction at point 'L', magnetic saturation is achieved.
- When ' H ' is ~~back~~ from 'L' to 'M', a similar curve EFGA is obtained.
- If we again start from 'G' the same curve GACDEFG is obtained once again.

→ The lagging of 'B' behind 'H' is known as Hysterisis.




Coupled circuit

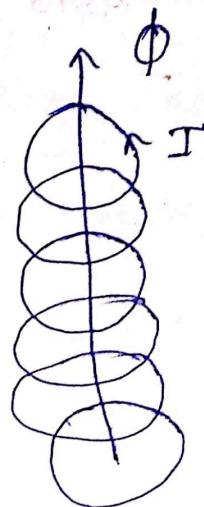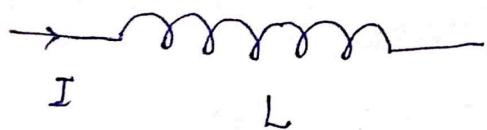

$$\text{Self Inductance} \Rightarrow L = \frac{N\phi}{i}$$

when a current changes in a circuit
the magnetic flux linking the same
circuit changes and an emf is induced
in the circuit.

$$V_L = L \frac{di}{dt}$$

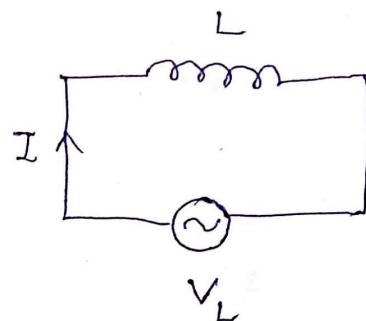

$$\Rightarrow V_L = L \frac{d}{dt} \left(\frac{N\phi}{L} \right)$$

$$\Rightarrow V_L = L \times \frac{N}{L} \times \frac{d\phi}{dt}$$

$$\Rightarrow V_L = N \frac{d\phi}{dt} \doteq L \frac{di}{dt}$$


$$\Rightarrow N \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$\Rightarrow N d\phi = L di$$

$$\boxed{L = N \frac{d\phi}{di}}$$

→ self - Inductance .

Mutual Inductance :-

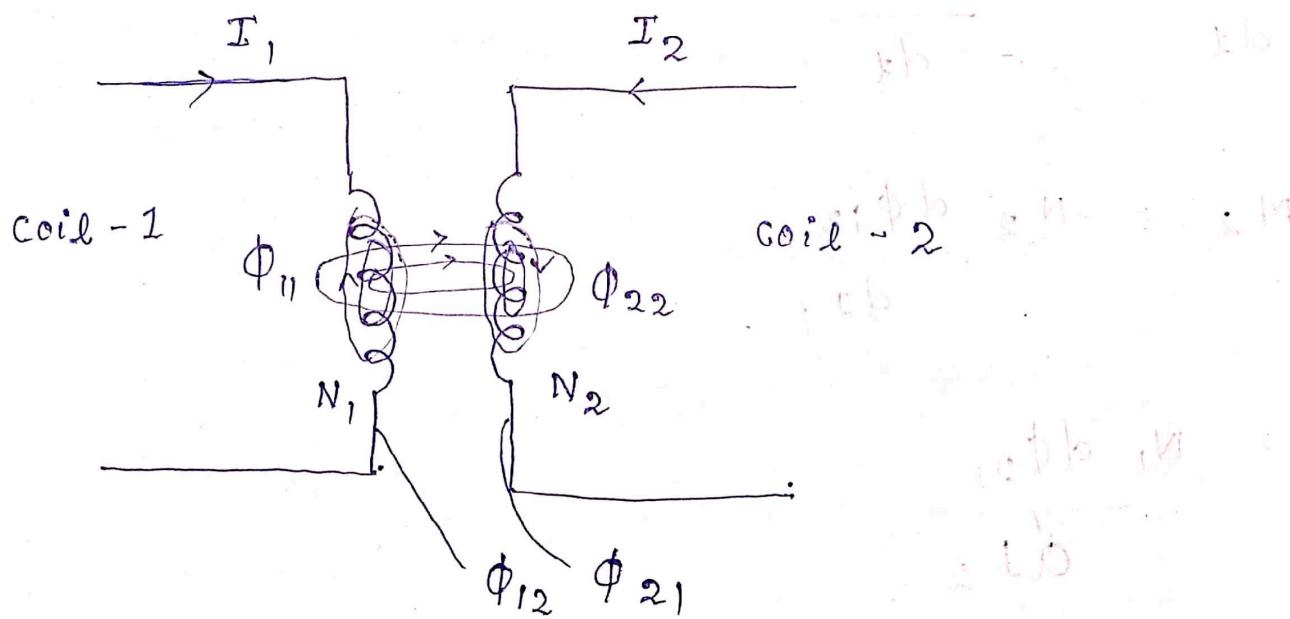


Let two coils carry a current of I_1 ,

and I_2 (alternating current). Each coil have leakage flux of ϕ_{11} and ϕ_{22} and mutual flux of ϕ_{12} and ϕ_{21} .

ϕ_{21} respectively.

$$V_{L_2} = \frac{N_2 d\phi_{12}}{dt}$$

$$= N_2 \frac{d}{dt} k I_1$$

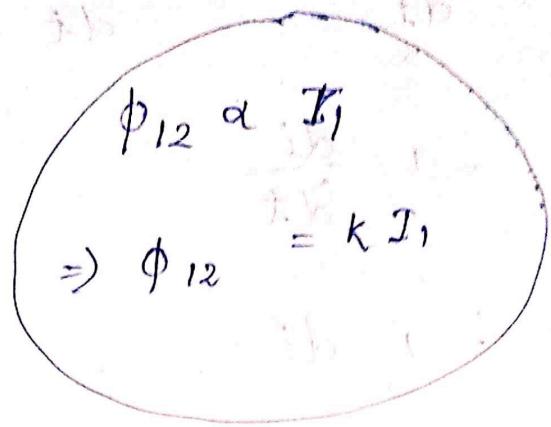

$$V_{L_2} = N_2 k \frac{dI_1}{dt}$$

$$V_{L_2} = M \frac{dI_1}{dt}$$

$$M \frac{dI_1}{dt} = N_2 \frac{d\phi_{12}}{dt}$$

$$\Rightarrow M_2 = N_2 \frac{d\phi_{12}}{dI_1}$$

$$M_1 = N_1 \frac{d\phi_{21}}{dI_2}$$

$$\Rightarrow M = N_2 \frac{\phi_{12}}{I_1}$$

$$M = N_1 \frac{\phi_{21}}{I_2}$$

→ Mutual - Inductance.

Co-efficient of coupling :-

It is defined as the fraction of total flux that links the coil.

$k = \text{co-efficient of coupling}$.

$$k = \frac{\Phi_{12}}{\Phi_1}$$

$$k = \frac{\Phi_{21}}{\Phi_2}$$

$$\Rightarrow \Phi_{21} = k\Phi_2$$

$$\Rightarrow \Phi_{12} = k\Phi_1$$

$$M = N_2 \frac{\Phi_{12}}{I_1} \quad M = N_1 \frac{\Phi_{21}}{I_2}$$

$$M^2 = N_2 \frac{\Phi_{12}}{I_1} \cdot N_1 \frac{\Phi_{21}}{I_2}$$


$$\Rightarrow M^2 = N_2 \frac{k\Phi_1}{I_1} \cdot N_1 \frac{k\Phi_2}{I_2}$$

$$\Rightarrow M^2 = k^2 \frac{N_1 \Phi_1}{I_1} \cdot \frac{N_2 \Phi_2}{I_2}$$

$$\Rightarrow M^2 = \kappa^2 L_1 L_2$$

$$\Rightarrow M = \kappa \sqrt{L_1 L_2}$$

series connection of coupled circuit :-

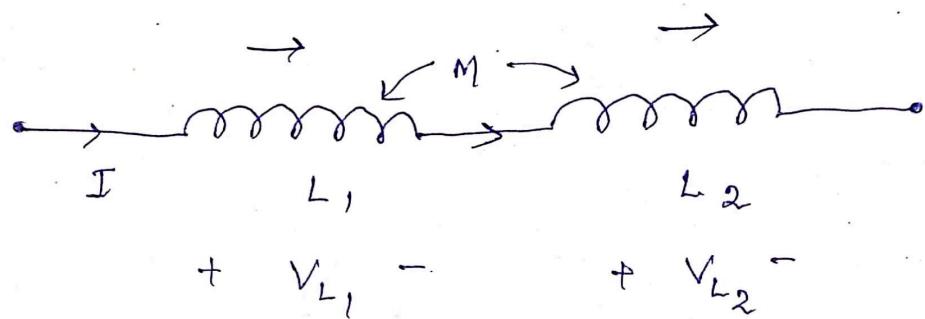

$$V_{L1} = L_1 \frac{dI}{dt} + M \frac{dI}{dt}$$

$$= (L_1 + M) \frac{dI}{dt}$$


$$V_{L2} = L_2 \frac{dI}{dt} + M \frac{dI}{dt}$$

$$= (L_2 + M) \frac{dI}{dt}$$

$$V_{L1} + V_{L2} = (L_1 + M) \frac{dI}{dt} + (L_2 + M) \frac{dI}{dt}$$

$$\Rightarrow V_L = (L_1 + L_2 + 2M) \frac{dI}{dt}$$

$$L = L_1 + L_2 + 2M$$

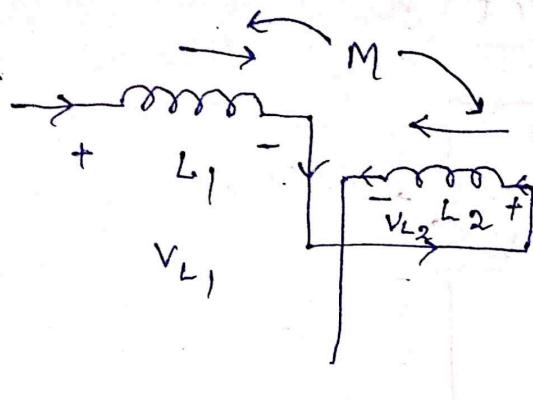

$$V_{L_1} = L_1 \frac{dI}{dt} - M \frac{dI}{dt}$$

$$= (L_1 - M) \frac{dI}{dt}$$

$$V_{L_2} = L_2 \frac{dI}{dt} - M \frac{dI}{dt}$$

$$= (L_2 - M) \frac{dI}{dt}$$

$$V_{L_1} + V_{L_2} = (L_1 - M) \frac{dI}{dt} + (L_2 - M) \frac{dI}{dt}$$


$$\Rightarrow V_L = (L_1 - M + L_2 - M) \frac{dI}{dt}$$

$$\Rightarrow V_L = (L_1 + L_2 - 2M) \frac{dI}{dt}$$

$$\Rightarrow L = L_1 + L_2 - 2M$$

Coupled circuit :-

Modeling of Coupled circuit :-

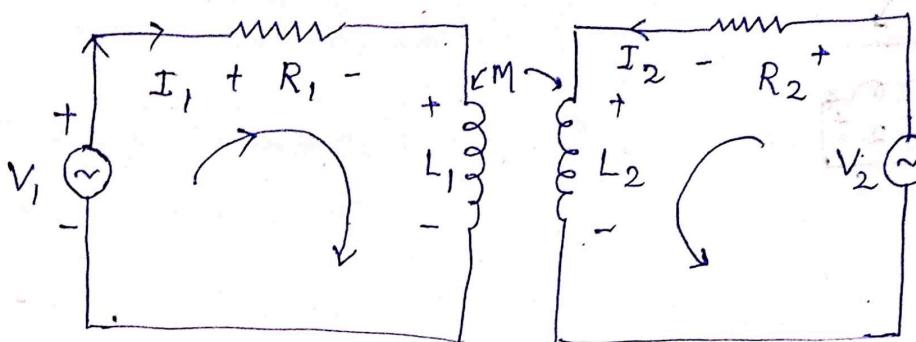

$$V_{L_1} = L_1 \frac{dI_1}{dt}$$

$$V_{L_2} = M \frac{dI_2}{dt}$$

$$V_1 - I_1 R_1 - L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} = 0$$

$$\Rightarrow V_1 = I_1 R_1 + L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}$$

$$V_2 = I_2 R_2 + L_2 \frac{dI_2}{dt} - M \frac{dI_1}{dt}$$

$$V_1 = I_1 R_1 + j\omega L_1 I_1 - j\omega M I_2$$

$$V_2 = I_2 R_2 + j\omega L_2 I_2 - j\omega M I_1$$



$$V_1 = (R_1 + j\omega L_1) I_1 - j\omega M I_2$$





$$V_2 = -j\omega M I_1 + (R_2 + j\omega L_2) I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_1 + j\omega L_1 & -j\omega M \\ -j\omega M & R_2 + j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Dot convention :-

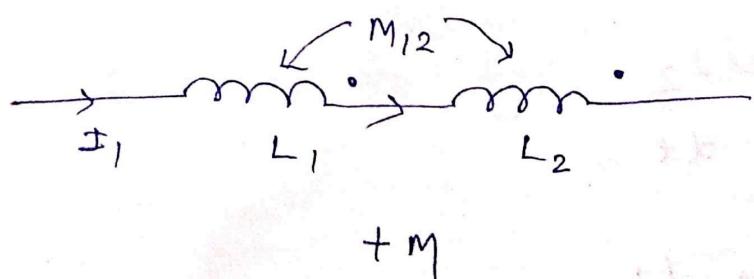
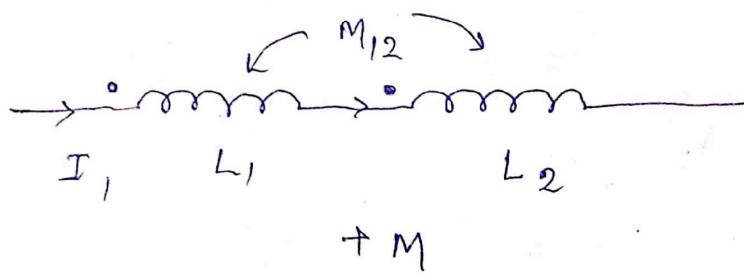
To determine the relative polarity of the induced voltage in the coupled coil, the coils are marked with dot. When current through each of the mutually coupled coils are going away from the dots or towards the dot, the mutual inductance is positive but when the current through the coils is leaving the dot for one coil and entering the other, the mutual inductance is negative.



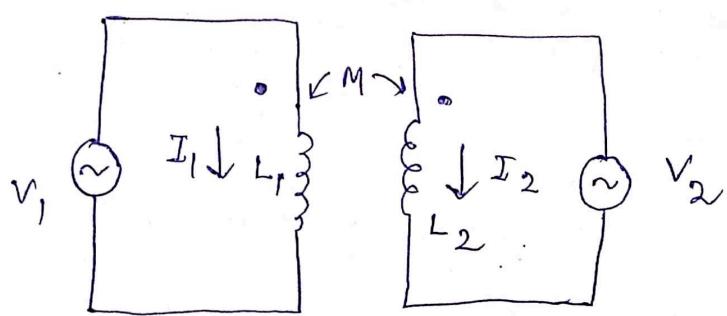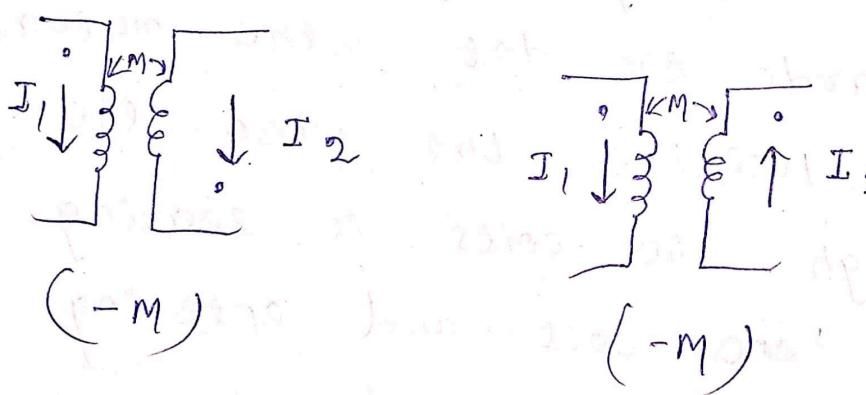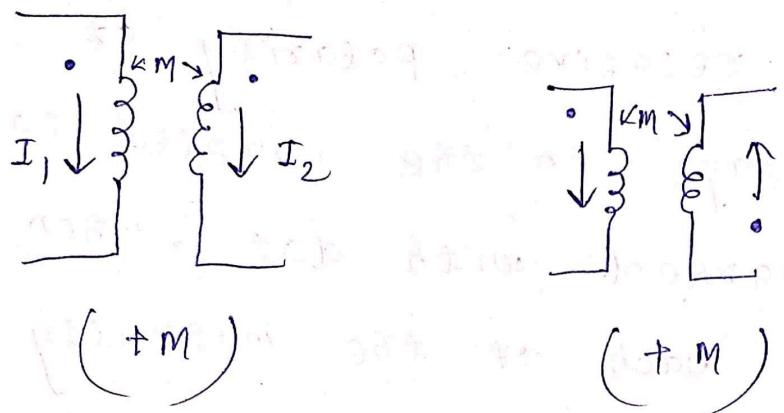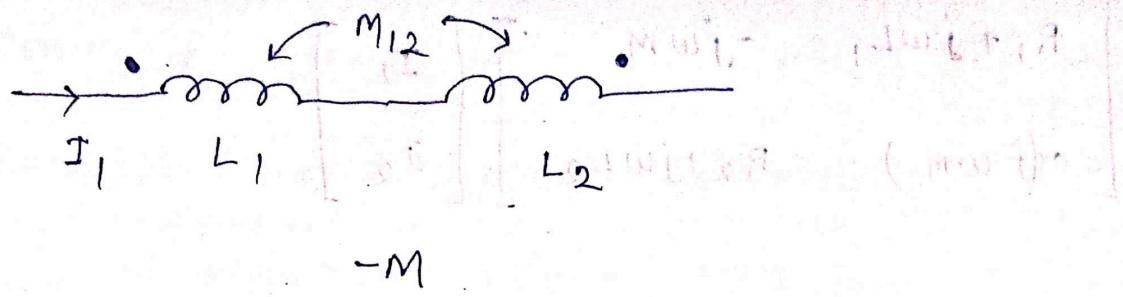

$$v_1 - L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt} = 0$$
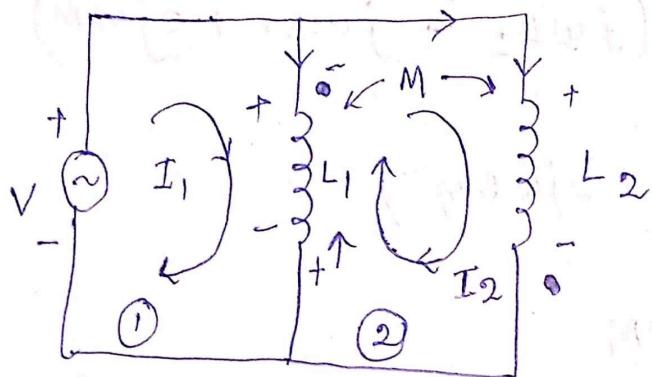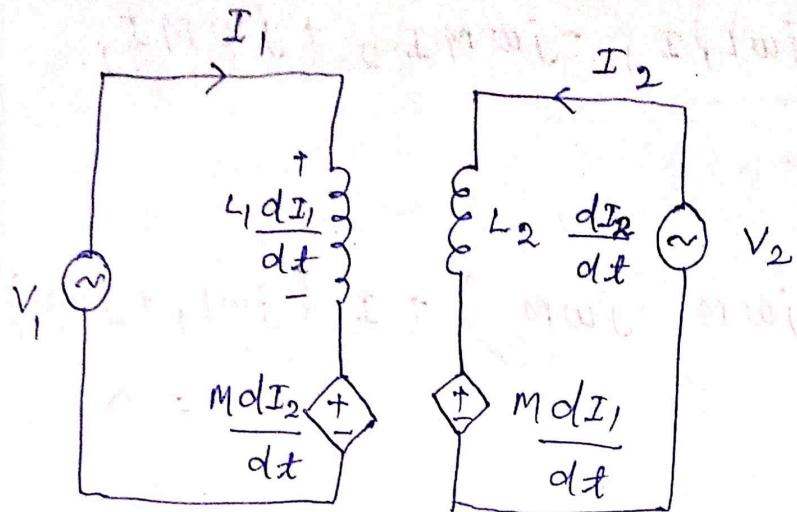
$$v_2 - L_2 \frac{dI_2}{dt} - M \frac{dI_1}{dt} = 0$$



$$V_1 - L_1 \frac{d(I_1 - I_2)}{dt} + M \frac{dI_2}{dt} = 0$$

$$V_1 - j\omega L_1 (I_1 - I_2) + j\omega M I_2 = 0$$

$$V_1 = j\omega L_1 (I_1 - I_2) - j\omega M I_2$$

$$= j\omega L_1 I_1 - j\omega L_1 I_2 - j\omega M I_2 \quad \text{--- (1)}$$

$$\begin{aligned} V_1 &= j\omega L_1 I_1 - I_2 (j\omega L_1 + j\omega M) \quad \text{--- (1)} \\ &- j\omega L_2 I_2 - j\omega L_1 (I_2 - I_1) - j\omega M (I_2 - I_1) \\ &\quad - j\omega M I_2 = 0 \end{aligned}$$

$$\Rightarrow -j\omega L_2 I_2 - j\omega L_1 I_2 + j\omega L_1 I_1 - j\omega M I_2 + j\omega M I_1$$

$$-j\omega M I_2 = 0$$

$$\Rightarrow I_2 (-j\omega L_2 - j\omega L_1 - j\omega M - j\omega M) + I_1 (j\omega L_1 + j\omega M) = 0$$

$$\Rightarrow I_1 (j\omega L_1 + j\omega M) = -I_2 (-j\omega L_2 - j\omega L_1 - 2j\omega M)$$

$$\Rightarrow I_1 (j\omega L_1 + j\omega M) = I_2 (j\omega L_2 + j\omega L_1 + 2j\omega M)$$

$$\Rightarrow I_1 = I_2 \underbrace{(j\omega L_2 + j\omega L_1 + 2j\omega M)}_{j\omega L_1 + j\omega M}$$

$$\Rightarrow I_2 = \left(\frac{j\omega L_1 + j\omega M}{j\omega L_2 + j\omega L_1 + 2j\omega M} \right) I_1$$

$$\Rightarrow I_2 = \left(\frac{j\omega (L_1 + M)}{j\omega (L_2 + L_1 + 2M)} \right) I_1$$

Putting value of I_2 in eqⁿ ①,

$$V_1 = j\omega L_1 I_1 - \frac{(L_1 + M)(j\omega L_1 + j\omega M)}{(L_2 + L_1 + 2M)} \times I_1$$


$$\Rightarrow V_1 = I_1 \left(j\omega L_1 - \frac{(L_1 + M)(j\omega L_1 + j\omega M)}{L_2 + L_1 + 2M} \right)$$

$$\Rightarrow \frac{V_1}{I_1} = j\omega \left(L_1 - \frac{L_1^2 + L_1 M + M L_1 + M^2}{L_2 + L_1 + 2M} \right)$$

$$\Rightarrow \frac{V_1}{j\omega I_1} = \frac{L_1 L_2 + L_1^2 + 2ML_1 - L_1^2 - 2ML_1 - M^2}{L_1 + L_2 + 2M}$$

$$\Rightarrow \text{Req } Z = \frac{V_1}{j\omega L_1} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} \quad (\text{opposing})$$
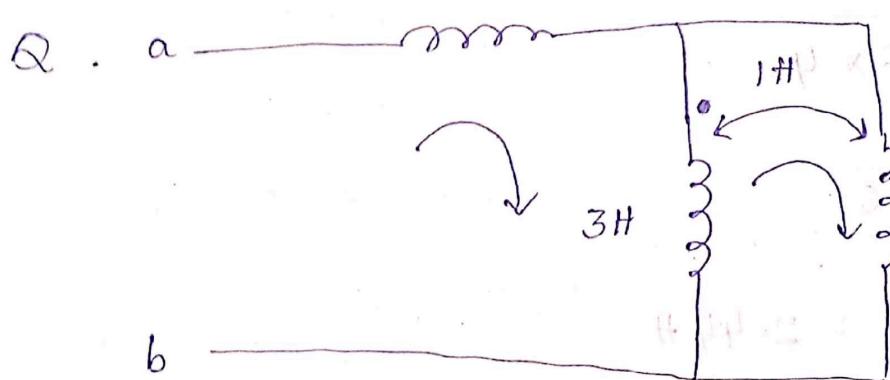
$$\boxed{\frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} \text{ (adding)}}$$




$$L_1 = 3H, \quad L_2 = 3H, \quad M = 1H$$

$$L = \frac{3 \times 3 - 1^2}{3 + 3 - 2 \times 1}$$

$$= \frac{9 - 1}{6 - 2}$$


$$= \frac{8}{4}$$

$$= 2H$$

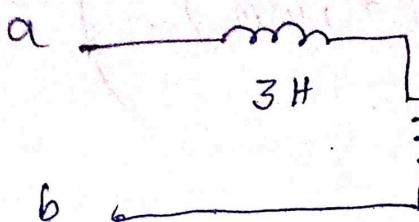

$$Leg = 3 + 2 = 5H \quad (\underline{\text{Ans}})$$

Q.

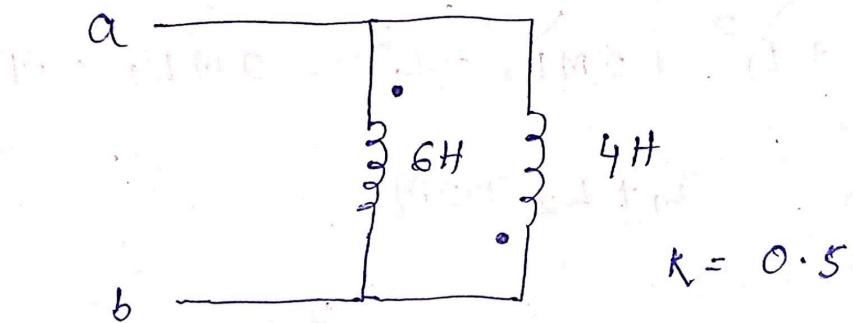

$$Leg = ?$$

$$\begin{aligned} M &= K \sqrt{L_1 L_2} \\ &= 0.5 \sqrt{6 \times 4} \\ &= \frac{1}{2} \times 2 \sqrt{6} \\ &= \sqrt{6} H = 2.44 H \end{aligned}$$

$$\begin{aligned} Leg &= \frac{6 \times 4 + 6}{6 + 4 + 2\sqrt{6}} = \frac{24 + 6}{10 + 2\sqrt{6}} \\ &= \frac{18}{10 + 2\sqrt{6}} = \frac{18}{14.88} \\ &= \frac{9}{5 + \sqrt{6}} H = 1.2 H \quad (\underline{\text{Ans}}) \end{aligned}$$

Q. Two coupled coil have self inductances
 $L_1 = 10 \times 10^{-3} \text{ H}$ and $L_2 = 20 \times 10^{-3} \text{ H}$.
The co-efficient of coupling $k = 0.75$.
Find the voltage in the second coil and flux of the 1st coil provided the second coil has 500 turns and the circuit current is given by $I_1 = 2 \sin 314 t \text{ A}$.

Sol' Given data,

$$L_1 = 10 \times 10^{-3} \text{ H}$$

$$L_2 = 20 \times 10^{-3} \text{ H}$$

$$k = 0.75$$

$$V_2 = ?$$

$$I_1 = 2 \sin 314 t$$

$$\begin{aligned}
M &= k \sqrt{L_1 L_2} \\
&= 0.75 \sqrt{10 \times 10^{-3} \times 20 \times 10^{-3}} \\
&= 0.75 \sqrt{200 \times 10^{-6}} \\
&= 0.75 \sqrt{2 \times 10^{-4}} \\
&= 0.75 \sqrt{2} \times 10^{-2} \\
&= 0.01 \text{ H}
\end{aligned}$$

$$V_2 = M \frac{dI}{dt}$$

$$= 0.01 \times \frac{d}{dt} (2 \sin 314t)$$

$$= 0.01 \times 2 \frac{d}{dt} \sin(314t)$$

$$= 0.02 \times \cos 314t \times 314$$

$$= 6.28 \cos 314t$$

$$L_1 = \frac{N_1 \Phi_1}{I_1}$$

$$M_2 = \frac{N_2 \Phi_{12}}{I_1}$$

$$M_2 = \frac{N_2 (\kappa \Phi_1)}{I_1}$$


$$M_2 = M_1 = M$$

$$\Rightarrow 0.01 = \frac{500 \times (0.75) \times \Phi_1}{2 \sin 314t}$$

$$\Rightarrow \Phi_1 = \frac{0.01 \times 2 \sin 314t}{500 \times 0.75}$$

$$\Rightarrow \phi_1 = 5.3 \times 10^{-5} \sin 314t$$

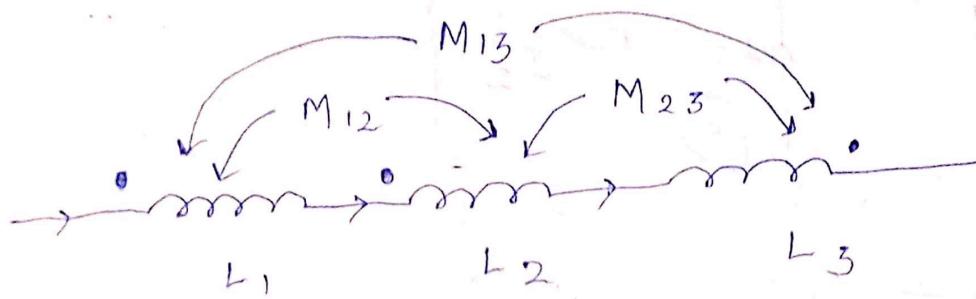Q. Find the total inductance of the three series connected coupled coil as shown in the figure.



$$L_1 = 1H$$

$$L_2 = 6H$$

$$L_3 = 3H$$

$$M_{12} = 2H$$

$$M_{23} = 4H$$

$$M_{13} = 5H$$

Solⁿ


$$L_1 + M_{12} - M_{13} + L_2 - M_{23} + M_{12} + L_3 - M_{23} - M_{13}$$

$$= 1 + 2 - 5 + 6 - 4 + 2 + 3 - 4 - 5$$

$$= 14 - 18$$

$$= -4 H$$

Q. Find the drop across R_L

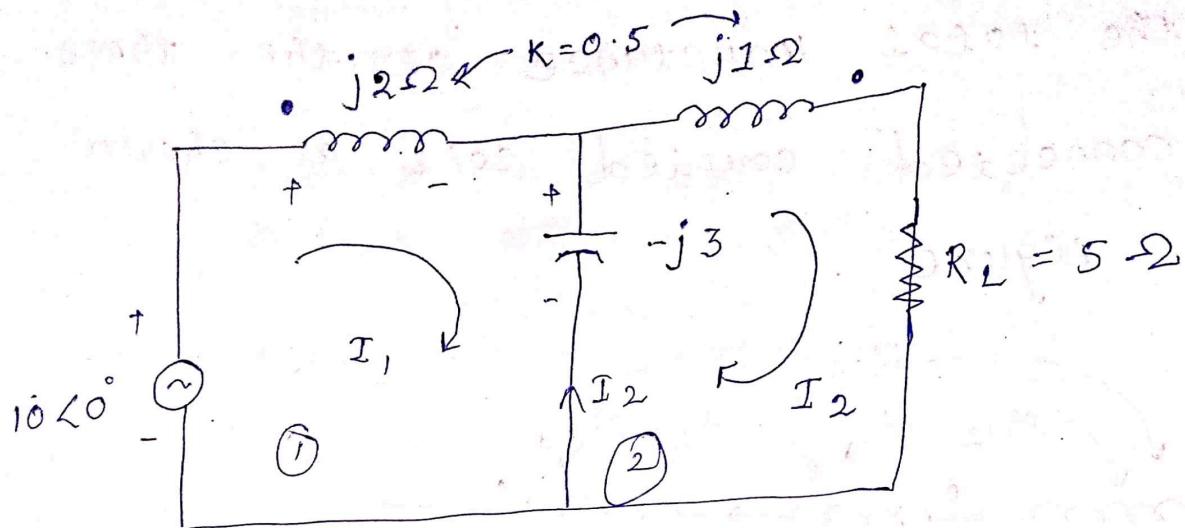

$$M = K \sqrt{L_1 L_2}$$

$$= 0.5 \sqrt{2 \times 1}$$

$$= 0.7 \text{ H}$$

for loop ①,

$$10 \angle 0^\circ = I_1(j2) - (I_1 - I_2)(-j3)$$

$$10 \angle 0^\circ = I_1(j2) + (I_1 - I_2)(-j3) - I_2(0.707j) \quad \text{--- } ①$$

for loop ②,

$$0 - I_2(j1) - I_2 \times 5 - (I_2 - I_1)(-j3) = 0$$

$$\Rightarrow 0 = I_2(j1) + I_2 \times 5 + (I_2 - I_1)(-j3)$$

$$-I_1(0.707j)$$

--- ②

$$\text{solving eq' } ①, \quad 10 L^0 = j_2 I_1 - j_3 I_1 + j_3 I_2 - j 0.707 I_2$$

$$10 L^0 = -j I_1 + 2.293 j I_2$$

solving eq' ②,

$$0 = j_1 I_2 + 5 I_2 - j_3 I_2 + j_3 I_1 - j 0.707 I_1$$

$$0 = -j_2 I_2 + 5 I_2 + j 2.293 I_1$$

$$0 = I_2(5 - j_2) + j 2.293 I_1$$

$$10 L^0 = -j I_1 + j 2.293 I_2 \quad — ③$$

$$0 = j 2.293 I_1 + (5 - j_2) I_2 \quad — ④$$

$$\begin{bmatrix} 10 L^0 \\ 0 \end{bmatrix} = \begin{bmatrix} -j_1 & j 2.293 \\ j 2.293 & 5 - j_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$I_2 = \frac{\begin{bmatrix} -j_1 & 10 L^0 \\ j 2.293 & 0 \end{bmatrix}}{\begin{bmatrix} -j_1 & j 2.293 \\ j 2.293 & 5 - j_2 \end{bmatrix}}$$

$$\begin{bmatrix} -j_1 & j 2.293 \\ j 2.293 & 5 - j_2 \end{bmatrix}$$

$$I_2 = \frac{(0 - 10 \angle 0^\circ (+j 2.293))}{-j 1(5-j 2) - (j 2.293)(j 2.293)}$$

$$= \frac{(0 - 10 \angle 0^\circ \times (2.293 \angle 90^\circ))}{(1 \angle -90^\circ)(5.385 \angle -21.80^\circ) - (2.293 \angle 90^\circ)}$$

$$(2.293 \angle 90^\circ)$$

$$= \frac{(0 - 10 \angle 0^\circ (0 + j 2.293))}{(0 - j 1)(5 - j 2) - (0 + j 2.293)(0 + j 2.293)}$$

$$\begin{bmatrix} 10 & L \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} -j1 & j2.293 \\ j2.293 & 5-j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 10+j0 \\ 0 \end{bmatrix} = \begin{bmatrix} -j1 & j2.293 \\ j2.293 & 5-j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} 10+j0 & j2.293 \\ j2.293 & 5-j2 \end{bmatrix}}{\begin{bmatrix} -j1 & j2.293 \\ j2.293 & 5-j2 \end{bmatrix}}$$

$$\begin{bmatrix} -j1 & j2.293 \\ j2.293 & 5-j2 \end{bmatrix}$$

$$= \frac{35.257849 - j20}{3.257849 - j5}$$

$$= \frac{58.765 - 19.897}{5.967 - 56.91}$$

$$= 9.8483 \angle 37.01^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \begin{bmatrix} -j1 & 10+j0 \\ j2.293 & 0 \end{bmatrix}$$

$$\begin{bmatrix} -j1 & j2.293 \\ j2.293 & 5-j2 \end{bmatrix}$$

$$\begin{bmatrix} AB - CD \\ AB - CD \end{bmatrix}$$

$$\begin{bmatrix} AB - CD \\ AB - CD \end{bmatrix}$$

$$= 0 - 22.93j$$

$$3.257849 - 5i$$

$$= 22.93 L-90$$

$$5.967711463 L-56.912903$$


$$= 3.842344 L-33.0871$$

$$V = I_2 R_L$$

$$= (3.842 L-33.087) (5 L)$$

$$= 19.21 L-33.087 V$$

Q.

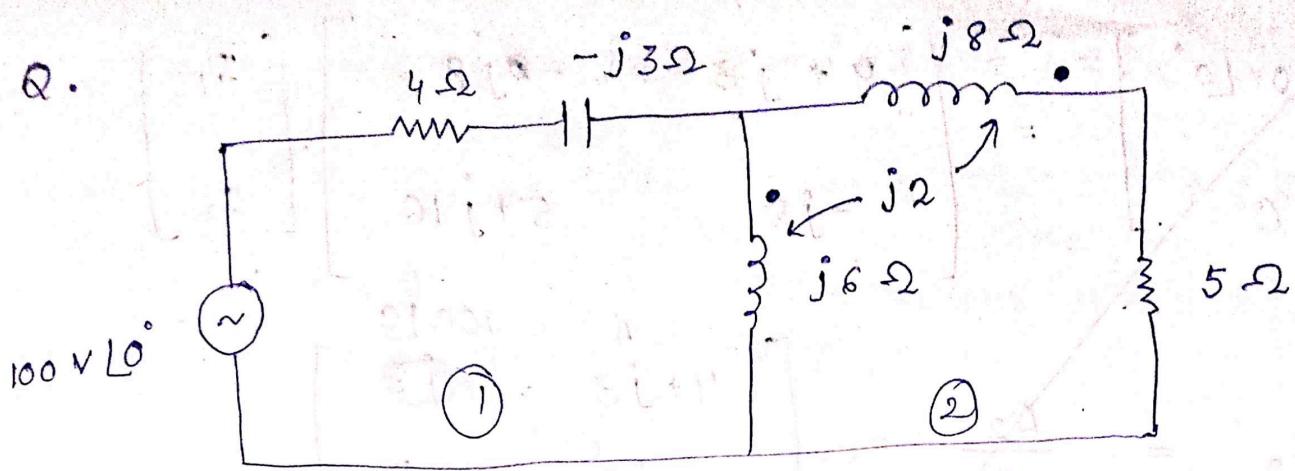

Determine the voltage drop across the
5 Ω resistor.

Sol?

$$100 \angle 0^\circ = 4I_1 + (-j3)I_1 + j6(I_1 - I_2) - j2I_2$$

$$\Rightarrow 100 \angle 0^\circ = 4I_1 - j3I_1 + j6I_1 - j6I_2 - j2I_2$$

$$\Rightarrow 100 \angle 0^\circ = I_1 (4 + j3) - 8jI_2$$

$$\Rightarrow 100 \angle 0^\circ = (4 + j3)I_1 - 8jI_2 \quad - \textcircled{1}$$

for loop ②,

$$0 = j8I_2 + 5I_2 + j6(I_2 - I_1) + j2(I_2 - I_1) + j2I_2$$

~~$$\Rightarrow 0 = j8I_2 + 5I_2 + j6I_2 - j6I_1 + j2I_2 - j2I_1$$~~

~~$$\Rightarrow 0 = -j8I_1 + (5 + 16j)I_2 \quad - \textcircled{2}$$~~

$$0 = j8I_2 + 5I_2 + j6I_2 - j6I_1 + j2I_2 - j2I_1$$

+ j2I_2

$$\Rightarrow 0 = j18I_2 + 5I_2 - j8I_1$$

$$\Rightarrow 0 = -j8I_1 + (5 + j18)I_2 \quad \text{--- (2)}$$

$$\begin{bmatrix} 100 & 0 \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow I_2 = \frac{\Delta_2}{\Delta_1} = \frac{\begin{bmatrix} A & D \\ 4 + j3 & 100 \\ C & B \\ -j8 & 0 \end{bmatrix}}{\begin{bmatrix} E & Y \\ 4 + j3 & -j8 \\ X & F \\ -j8 & 5 + j18 \end{bmatrix}}$$

$$= \frac{AB - CD}{EF - XY}$$

$$= \frac{j800}{30 + j87}$$

$$= 8 \cdot 2182 + j2 \cdot 8338$$


$$= 8 \cdot 69305 \boxed{19 \cdot 025}$$

$$V = I_2 \times 5 + 1.20 \text{ (neglecting ESR)}$$

$$= 8.69305 \angle 19.025^\circ \quad (5 \angle 0^\circ)$$

$$= 43.465 \angle 19.025^\circ$$

Q.

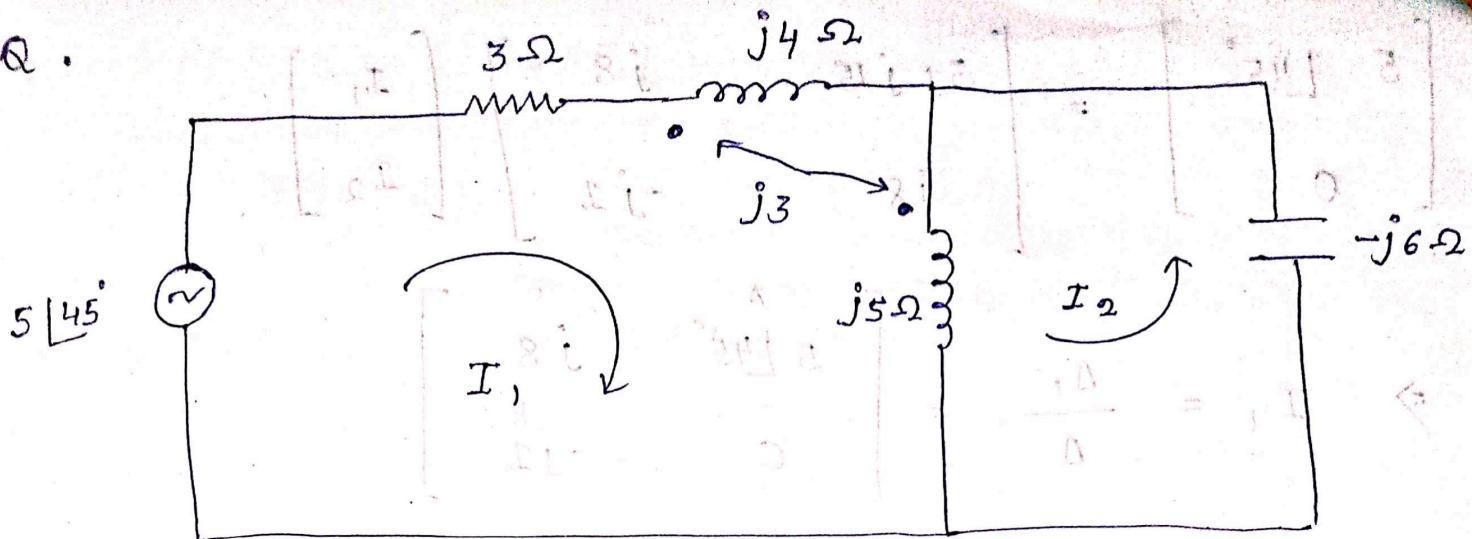

for loop ①,

$$5\angle 45^\circ = 3I_1 + j4I_1 + j5(I_1 + I_2) + j3(I_1 + I_2) + j3I_1$$

$$\Rightarrow 5\angle 45^\circ = 3I_1 + j4I_1 + j5I_1 + j5I_2 + j3I_1 + j3I_2 + j3I_1$$

$$\Rightarrow 5\angle 45^\circ = 3I_1 + 15jI_1 + 8jI_2$$

$$\Rightarrow 5\angle 45^\circ = (3 + 15j)I_1 + 8jI_2 \quad \text{--- } ①$$

$$\Rightarrow 5\angle 45^\circ = (3 + j15)I_1 + j8I_2 \quad \text{--- } ①$$

for loop ②,

$$0 = -j6I_2 + j5(I_2 + I_1) + j3I_1$$

$$\Rightarrow 0 = -j6I_2 + j5I_2 + j5I_1 + j3I_1$$

$$\Rightarrow 0 = j8I_1 - j2I_2 \quad \text{--- } ②$$

$$\begin{bmatrix} 5 & 5 \angle 45^\circ \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 3 + j15 & j8 \\ j8 & -j1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{bmatrix} A & 0 \\ C & -j1 \end{bmatrix}}{\begin{bmatrix} 3 + j15 & j8 \\ j8 & -j1 \end{bmatrix}}$$

$$AB - CD$$

$$EF - XY$$

$$= 3 \cdot 5355 - 3 \cdot 5355 j$$

$$79 - 3j$$

$$= 0.04638 - 0.04299 j$$

$$= 0.0632 \quad \boxed{-42.827}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} A & 3+j15 & 5[45^\circ] \\ C & j8 & B \\ 0 & 0 & 0 \end{bmatrix}}{\begin{bmatrix} 3+j15 & j8 \\ X & F \\ j8 & -j1 \end{bmatrix}}$$

$$= AB - CD$$

$$EF - XY$$


$$= 28.2842 - 28.2842 j$$

$$79 - 3j$$

$$= 0.37108 - 0.34393 j$$

$$= 0.50595 \quad \boxed{-42.8254}$$

Q.

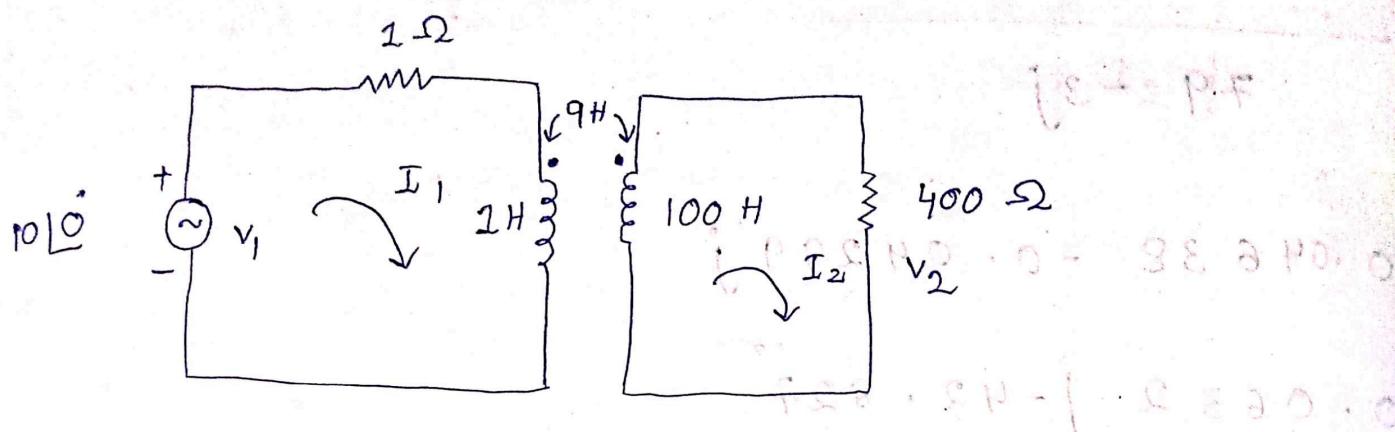

Calculate the ratio of the output voltage across 400 Ω resistor to the source voltage for the circuit shown in the figure.

$$\omega = 10 \text{ rad/sec}$$

Sol'

$$L_1 = 1 \text{ H}$$

$$X_{L_1} = \omega L_1$$

$$= 10 \times 1$$

$$= 10 \Omega$$

$$L_2 = 100 \text{ H}$$

$$X_{L_2} = \omega L_2$$

$$= 1000 \Omega$$

$$X_M = \omega M = 10 \times 9 = 90 \Omega$$

$$\frac{V_2}{V_1} = \frac{I_2 \times 400}{V_1}$$

for loop ①,

$$10 \angle 0^\circ = i_1 \times I_1 + j 10 I_1 - j 90 I_2$$

$$\Rightarrow 10 \angle 0^\circ = (1 + j 10) I_1 - j 90 I_2 \quad \text{--- } ①$$

for loop ②,

$$0 = 400 I_2 + j 1000 I_2 - j 90 I_1$$

$$\Rightarrow 0 = -j 90 I_1 + (400 + j 1000) I_2 \quad \text{--- } ②$$

$$\begin{bmatrix} 10 \angle 0^\circ \\ 0 \end{bmatrix} = \begin{bmatrix} 1 + j 10 & -j 90 \\ -j 90 & 400 + j 1000 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} 1 + j 10 & 10 \angle 0^\circ \\ -j 90 & 0 \end{bmatrix}}{\begin{bmatrix} 1 + j 10 & -j 90 \\ -j 90 & 400 + j 1000 \end{bmatrix}}$$


$$= \frac{j 900}{-1500 + j 5000}$$

$$= 0.1651376 - j 0.0495412$$

$$= 0.1724086 \angle -16.699218^\circ$$



$$\begin{aligned}
 \frac{V_2}{V_1} &= \frac{I_2 \times 400}{V_1} \\
 &= \frac{(0.1724086 L^{-16.699218}) \times 400}{10 L^0} \\
 &= \frac{68.96344 L^{-16.699218}}{10 L^0} \\
 &= 6.60550046246 - j 1.98164684208 \\
 &= 6.896344 L^{-16.699218} \quad (\text{Ans})
 \end{aligned}$$

Q.

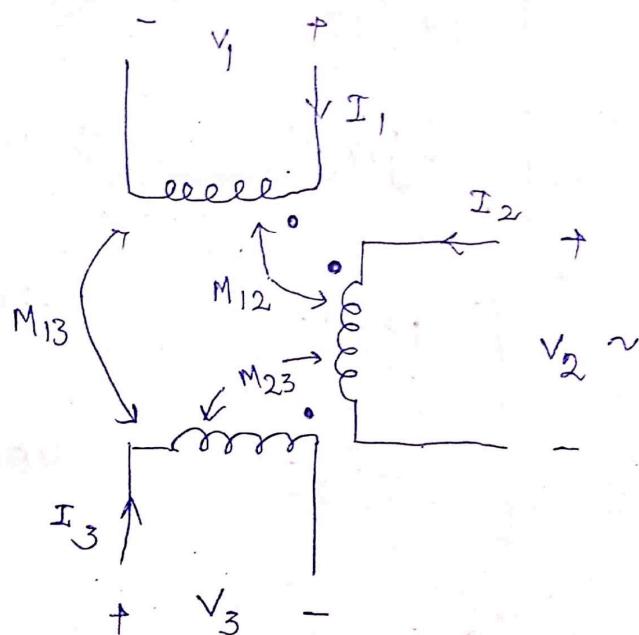

Find V_1 , V_2 and V_3 ?

Q.

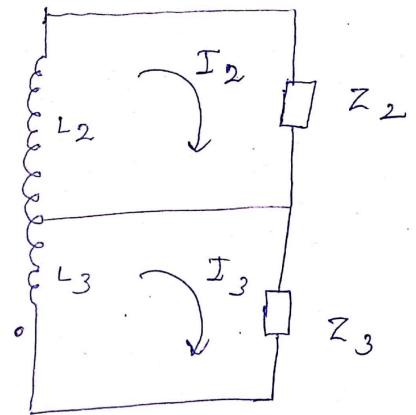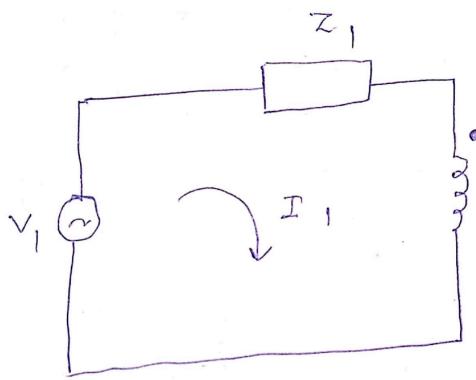


Find the mesh equation.

Circuit element and analysis :-



Circuit

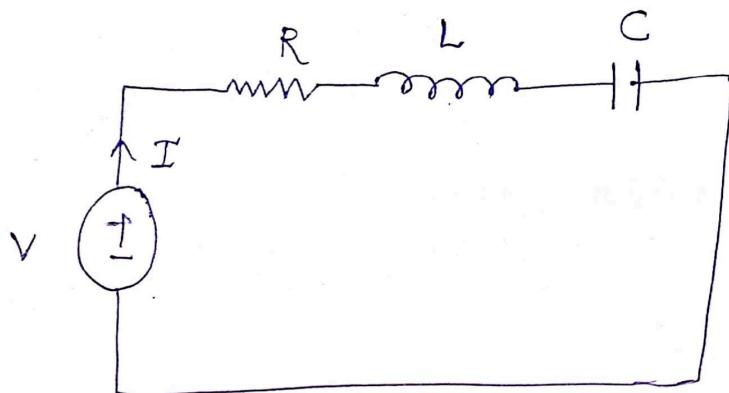circuit is a closed conducting path through which an electric current flows. It consists of active and passive element.





Linear circuit :-

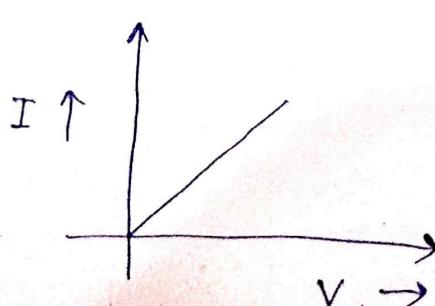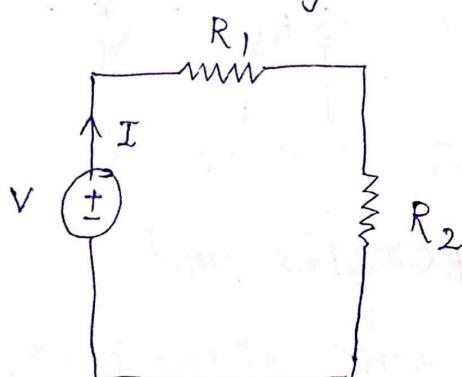A linear circuit is one whose parameters are constant with time and they do not change with voltage or current and the circuit obeys ohm's law.



Non-linear circuit :-

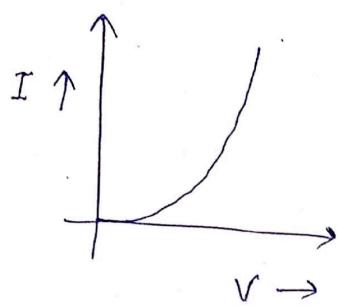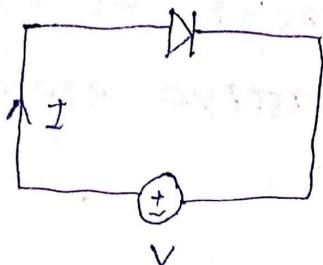It is that circuit whose parameters changes with voltage or current.




Bilateral Network :-



A bilateral circuit is one whose properties and characteristics are the same in either direction.

Ex :~ Transmission line

Unilateral Network :-

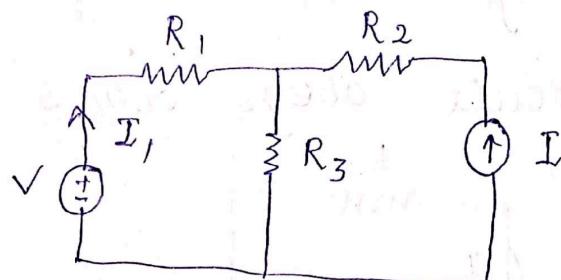
It is the circuit whose properties and characteristics changes with the direction of its operation.



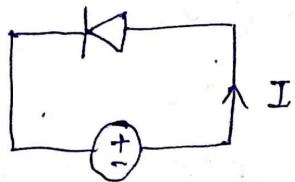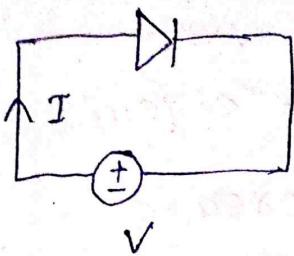


Passive Network :-

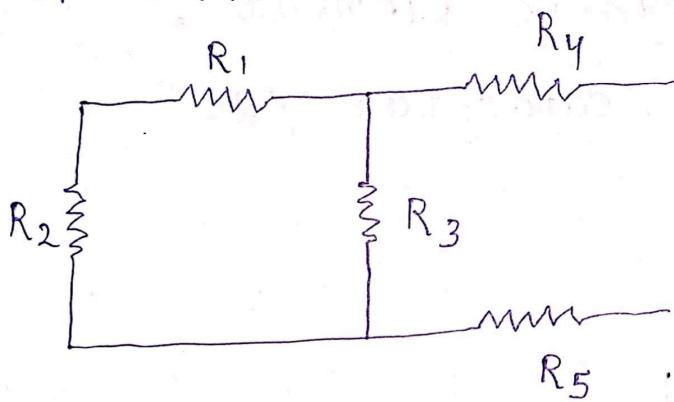It is the network which contain no source of emf.



Active Network :-

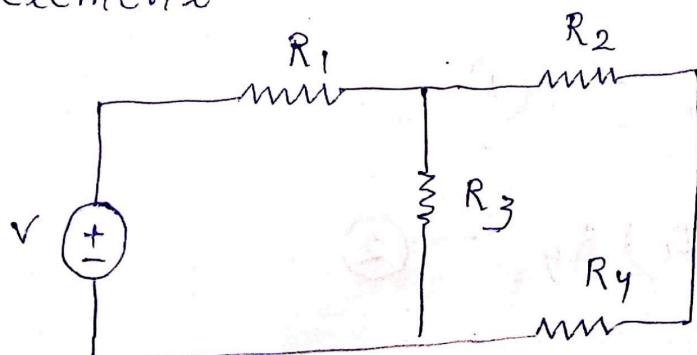It is a network which contain one or more than source of emf with passive element.



Active element :-

An active element is defined as the circuit component which can increase or decrease the energy level of a signal passing through it.


Ex :- Transistor, OP-Amp, Battery etc.

Passive element :-

Any circuit element which only consumes the power is called passive element.


Ex :- Resistor, Inductor, capacitor etc.

Mesh analysis :-

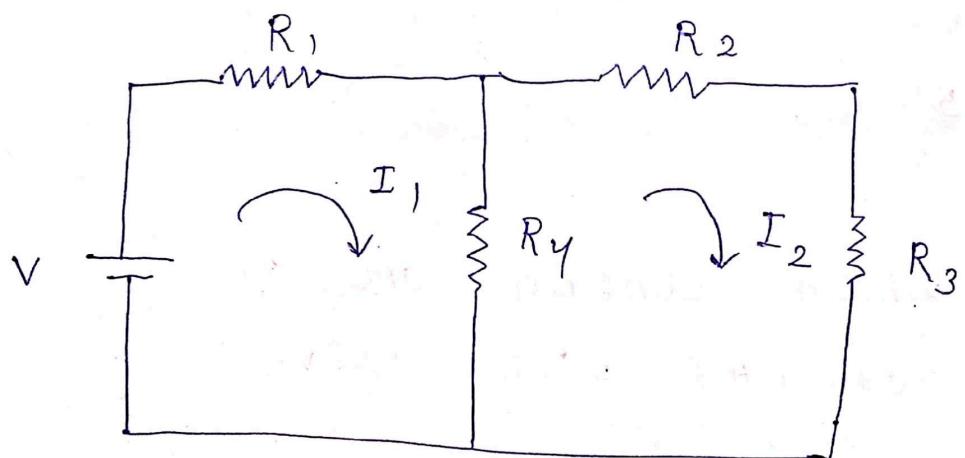

$$V = I_1 R_1 + (I_1 - I_2) R_y \quad \text{--- (1)}$$
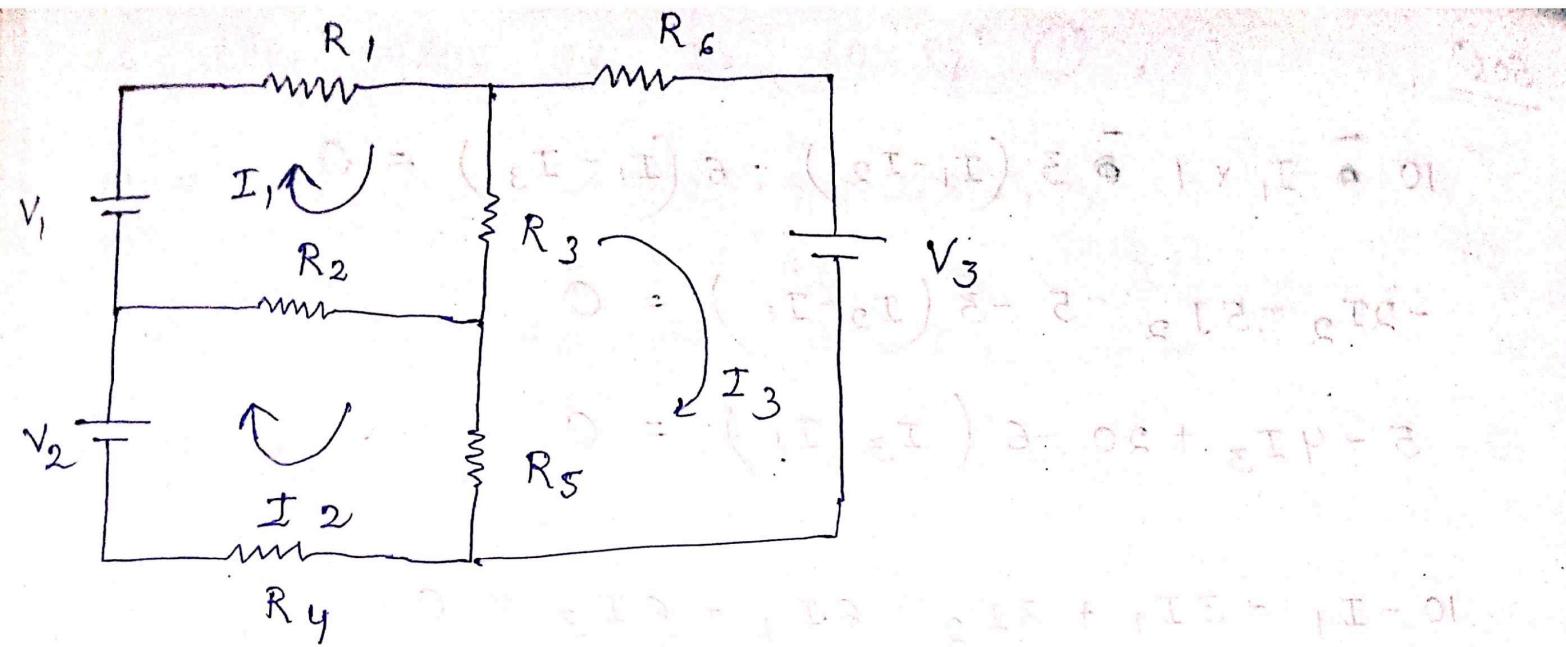
$$0 = I_2 R_2 + I_2 R_3 + (I_2 - I_1) R_y \quad \text{--- (2)}$$




$$V_1 = I_1 R_1 + (I_1 - I_3) R_3 + (I_1 - I_2) R_2$$

$$V_2 = (I_2 - I_1) R_2 + (I_2 - I_3) R_5 + I_2 R_4$$

$$-V_3 = (I_3 - I_2) R_5 + (I_3 - I_1) R_3 + I_3 R_6$$

Q.

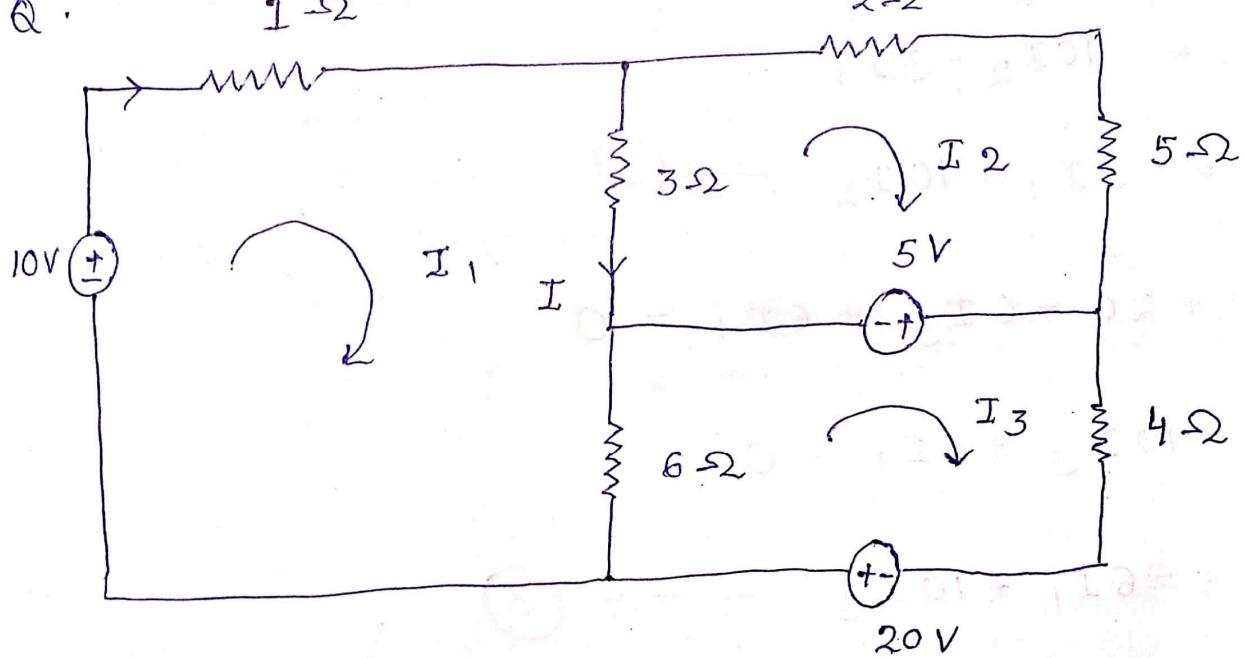

Determine current I using mesh analysis.

Solⁿ

$$10 - I_1 + 1 - 3(I_1 - I_2) - 6(I_1 - I_3) = 0$$

$$-2I_2 - 5I_2 - 5 - 3(I_2 - I_1) = 0$$

$$5 - 4I_3 + 20 - 6(I_3 - I_1) = 0$$

$$10 - I_1 - 3I_1 + 3I_2 - 6I_1 + 6I_3 = 0$$

$$10 - 10I_1 + 3I_2 + 6I_3 = 0$$

$$10 = 10I_1 - 3I_2 - 6I_3 \quad \text{--- (1)}$$

$$-2I_2 - 5I_2 - 5 - 3I_2 + 3I_1 = 0$$

$$\Rightarrow -10I_2 + 3I_1 - 5 = 0$$

$$\Rightarrow -5 = 10I_2 - 3I_1$$

$$\Rightarrow 5 = 3I_1 - 10I_2 \quad \text{--- (2)}$$

$$5 - 4I_3 + 20 - 6I_3 + 6I_1 = 0$$

$$\Rightarrow 25 - 10I_3 + 6I_1 = 0$$

$$\Rightarrow 25 = -6I_1 + 10I_3 \quad \text{--- (3)}$$

$$\Rightarrow 25 + 6I_1 = 10I_3$$

$$\Rightarrow I_3 = \frac{25 + 6I_1}{10}$$

$$\Rightarrow I_3 = 2.5 + 0.6I_1$$

put the value of I_3 in eq? ①

$$10 = 10I_1 - 3I_2 - 6(2.5 + 0.6I_1)$$

$$\Rightarrow 10 = 10I_1 - 3I_2 - 15 - 3.6I_1$$

$$\Rightarrow 10 + 15 = 6.4I_1 - 3I_2$$

$$\Rightarrow [25 = 6.4I_1 - 3I_2] \times 10 \quad \text{--- (4)}$$

$$[5 = 3I_1 - 10I_2] \times 3$$

$$\Rightarrow 250 = 64I_1 - 30I_2 \quad \text{--- (5)}$$

$$15 = 9I_1 - 30I_2 \quad \text{--- (6)}$$

Subtracting eq? (6) from eq? (5);

$$235 = 55I_1$$

$$\Rightarrow I_1 = 4.272$$

$$15 = 9(4.272) - 30I_2$$

$$\Rightarrow 30I_2 = 23.448$$

$$\Rightarrow I_2 = \frac{23.448}{30}$$

$$= 0.7816$$

$$I = I_1 - I_2$$

$$= 4.272 - 0.7816$$

$$= 3.4904 \text{ Amp}$$

$$\begin{bmatrix} 10 \\ 5 \\ 25 \end{bmatrix} = \begin{bmatrix} 10 & -3 & -6 \\ 3 & -10 & 0 \\ -6 & 0 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta}$$


$$= \begin{bmatrix} 10 & -3 & -6 \\ 5 & -10 & 0 \\ 25 & 0 & 10 \end{bmatrix}$$

$$\begin{bmatrix} 10 & -3 & -6 \\ 3 & -10 & 0 \\ -6 & 0 & 10 \end{bmatrix}$$

$$= \frac{10(-100) + 3(50 - 0) - 6(0 + 250)}{1000}$$


$$= \frac{-1000 + 150 - 1500}{1000}$$

$$= \frac{-2350}{1000}$$

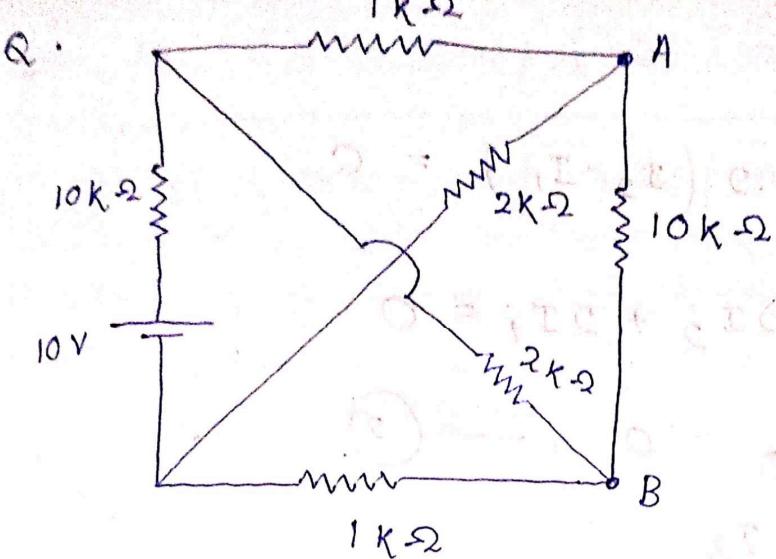

find the voltage across $10\text{k}\Omega$ resistor at terminal AB as shown in the figure.

Sol'

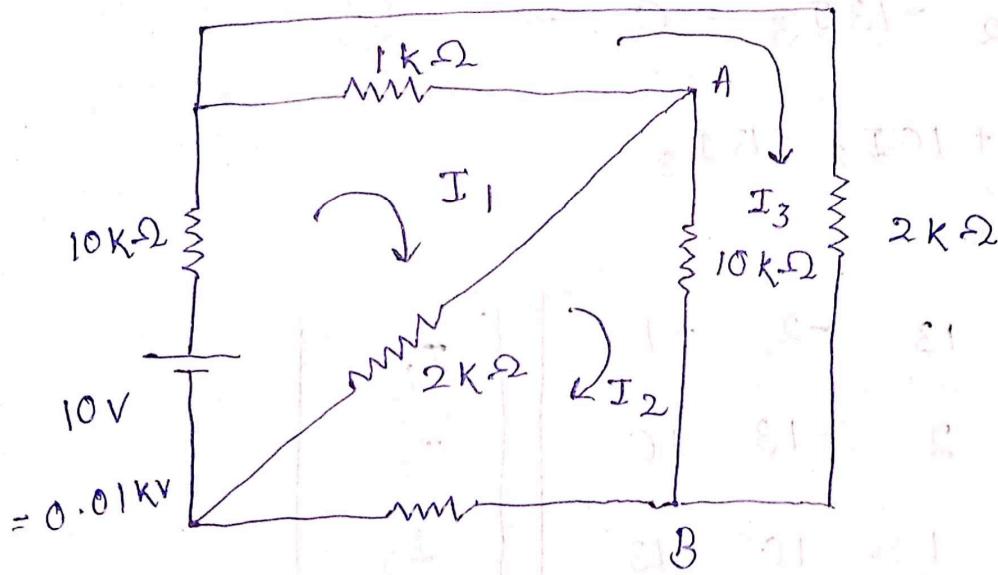

for loop ①,

$$0.01 - 10I_1 - 2(I_1 - I_3) - 2(I_1 - I_2) = 0$$

$$\Rightarrow 0.01 - 10I_1 - I_1 + I_3 - 2I_1 + 2I_2 = 0$$

$$\Rightarrow 0.01 - 13I_1 + 2I_2 + I_3 = 0$$

$$\Rightarrow 0.01 = 13I_1 - 2I_2 - I_3 \quad \text{--- ①}$$

for loop (2),

$$-10(I_2 - I_3) - I_2 \cdot 1 - 2(I_2 - I_1) = 0$$

$$\Rightarrow -10I_2 + 10I_3 - I_2 - 2I_2 + 2I_1 = 0$$

$$\Rightarrow 2I_1 - 13I_2 + 10I_3 = 0 \quad \text{--- (2)}$$

$$\Rightarrow 0 = 2I_1 - 13I_2 + 10I_3$$

for loop (3)

$$-2I_3 - 10(I_3 - I_2) - 1(I_3 - I_1) = 0$$

$$\Rightarrow -2I_3 - 10I_3 + 10I_2 - I_3 + I_1 = 0$$

$$\Rightarrow I_1 + 10I_2 - 13I_3 = 0 \quad \text{--- (3)}$$

$$\Rightarrow 0 = I_1 + 10I_2 - 13I_3$$

$$\begin{bmatrix} 0.01 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 13 & -2 & -1 \\ 2 & -13 & 10 \\ 1 & 10 & -13 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{bmatrix} 13 & 0.01 & -1 \\ 2 & 0 & 10 \\ 1 & 0 & -13 \end{bmatrix}}{\begin{bmatrix} 13 & -2 & -1 \\ 2 & -13 & 10 \\ 1 & 10 & -13 \end{bmatrix}}$$

$$\begin{bmatrix} 13 & -2 & -1 \\ 2 & -13 & 10 \\ 1 & 10 & -13 \end{bmatrix}$$

$$= \frac{13(0) - 0.01(-26-10) - 1(0)}{13(169-100) + 2(-26-10) - 1(20+13)}$$

$$= \frac{0 + 0.36 - 0}{897 - 72 - 33}$$

$$= \frac{0.36}{792}$$

$$= \frac{4.545}{10000}$$

$$= 0.0004545 \text{ KAMP}$$

$$= 0.4545 \text{ AMP}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{bmatrix} 13 & -2 & 0.01 \\ 2 & -13 & 0 \\ 1 & 10 & 0 \end{bmatrix}}{\begin{bmatrix} 13 & -2 & -1 \\ 2 & -13 & 10 \\ 1 & 10 & -13 \end{bmatrix}}$$

$$\frac{\begin{bmatrix} 13 & -2 & -1 \\ 2 & -13 & 10 \\ 1 & 10 & -13 \end{bmatrix}}{\begin{bmatrix} 13 & -2 & -1 \\ 2 & -13 & 10 \\ 1 & 10 & -13 \end{bmatrix}}$$

$$= \frac{13(0) + 2(0) + 0.01(20+13)}{792}$$

$$= \frac{0.33}{792}$$

$$= 0.00041 \text{ KA}$$

$$= 0.41 \text{ Amp}$$

$$V = IR$$

$$= (I_2 - I_3) \times 10000$$


$$= (0.045 - 0.41) \times 10000$$

$$= 0.04 \times 1000$$

$$= 400 \text{ volt}$$

super mesh analysis :-

Q.

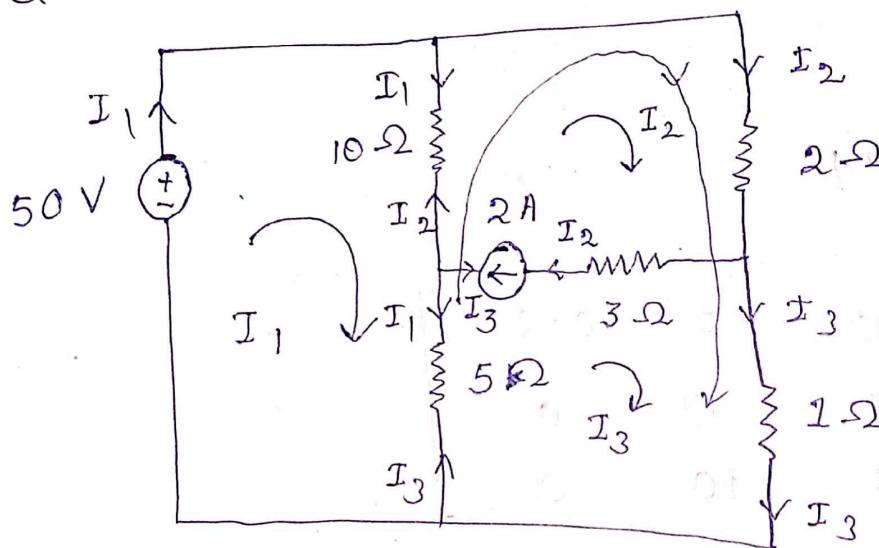

What is the voltage across 1 ohm resistor.

$$50 - 10(I_1 - I_2) - 5(I_1 - I_3) = 0$$

$$\Rightarrow 50 - 10I_1 + 10I_2 - 5I_1 + 5I_3 = 0$$

$$\Rightarrow 50 - 15I_1 + 10I_2 + 5I_3 = 0$$

$$\Rightarrow 50 = 15I_1 - 10I_2 - 5I_3 \quad \text{--- (1)}$$

$$-2I_2 - I_3 - 5(I_3 - I_1) - 10(I_2 - I_1) = 0$$

$$\Rightarrow -2I_2 - I_3 - 5I_3 + 5I_1 - 10I_2 + 10I_1 = 0$$

$$\Rightarrow 15I_1 - 12I_2 - 6I_3 = 0$$

$$\Rightarrow 0 = 15I_1 - 12I_2 - 6I_3 \quad \text{--- (2)}$$

$$I_2 + 2 - I_3 = 0$$

$$\Rightarrow 2 = I_3 - I_2 \quad \text{--- (3)}$$

$$\Rightarrow 2 = -I_2 + I_3 \quad \text{--- (3)}$$

$$\Rightarrow I_3 = 2 + I_2 \quad \text{--- (1) and}$$

put the value of I_3 in eqⁿ (2)

$$50 = 15I_1 - 10I_2 - 5(2 + I_2)$$

$$\Rightarrow 50 = 15I_1 - 10I_2 - 10 - 5I_2$$

$$\Rightarrow 50 + 10 = 15I_1 - 15I_2$$

$$\Rightarrow 60 = 15I_1 - 15I_2 \quad \text{--- (4)}$$

$$0 = 15I_1 - 12I_2 - 6(2 + I_2)$$

$$\Rightarrow 0 = 15I_1 - 12I_2 - 12 - 6I_2$$

$$\Rightarrow 0 + 12 = 15I_1 - 18I_2$$

$$\Rightarrow 12 = 15I_1 - 18I_2 \quad \text{--- (5)}$$

Subtracting eqⁿ (5) from (4),

$$\Rightarrow 48 = 3I_2$$

$$\Rightarrow I_2 = 16 \text{ Amp}$$

Putting the value of I_2 in eqⁿ (4),

$$\Rightarrow 60 = 15I_1 - 15 \times 16$$


$$\Rightarrow 300 = 15I_1$$

$$\Rightarrow I_1 = 20 \text{ Amp}$$

$$\begin{aligned}
 I_3 &= 2 + I_2 \\
 &= 2 + 16 \\
 &= 18 \text{ Amp}
 \end{aligned}$$

$$\begin{aligned}
 V &= I_3 \times 1 \\
 &= 18 \times 1 \\
 &= 18 \text{ volt} \quad (\text{Ans})
 \end{aligned}$$

Q.

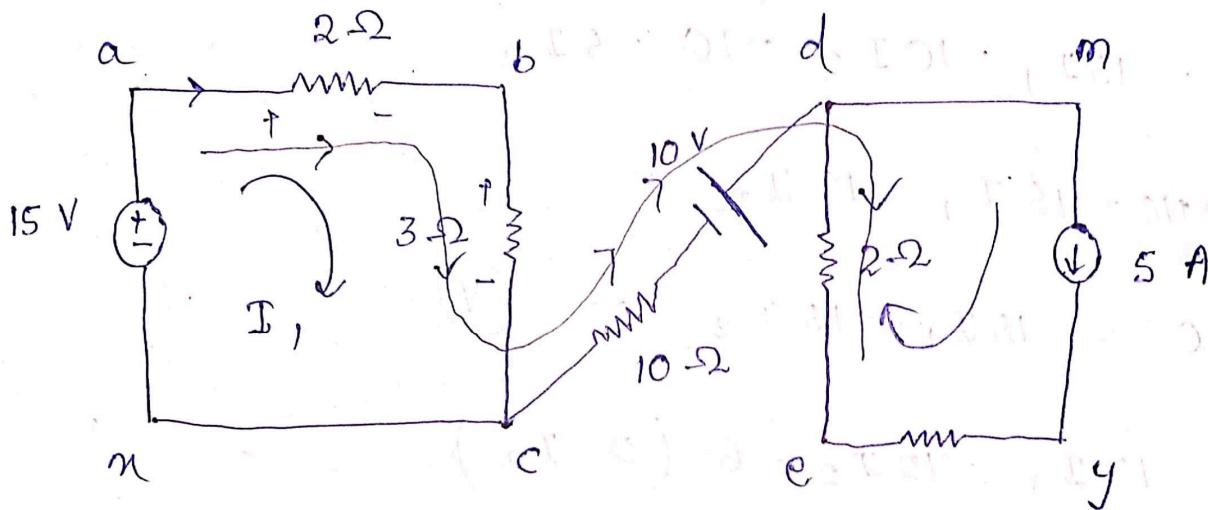

Find the voltage drop between the terminal α and e.

Sol'

$$15 - 2I_1 - 3I_1 = 0$$

$$\Rightarrow 15 = 5I_1$$

$$\Rightarrow I_1 = 3 \text{ Amp}$$

$$V_{ae} = V_a \pm V_{2\Omega} \pm V_{3\Omega} \pm V_{10\Omega} \pm 10V \pm V_{2\Omega} - V_e = 0$$


$$V_a \pm V_{2\Omega} \pm V_{3\Omega} \pm V_{10\Omega} \pm 10V \pm V_{2\Omega} - V_e = 0$$

$$V_a - 3 \times 2 - 3 \times 3 \pm 0 + 10 + 5 \times 2 - V_e = 0$$

$$V_a - V_e = +6 + 9 \quad - \quad - \quad 10 \quad 10$$

$$V_{ae} = +15 \quad - \quad 20$$
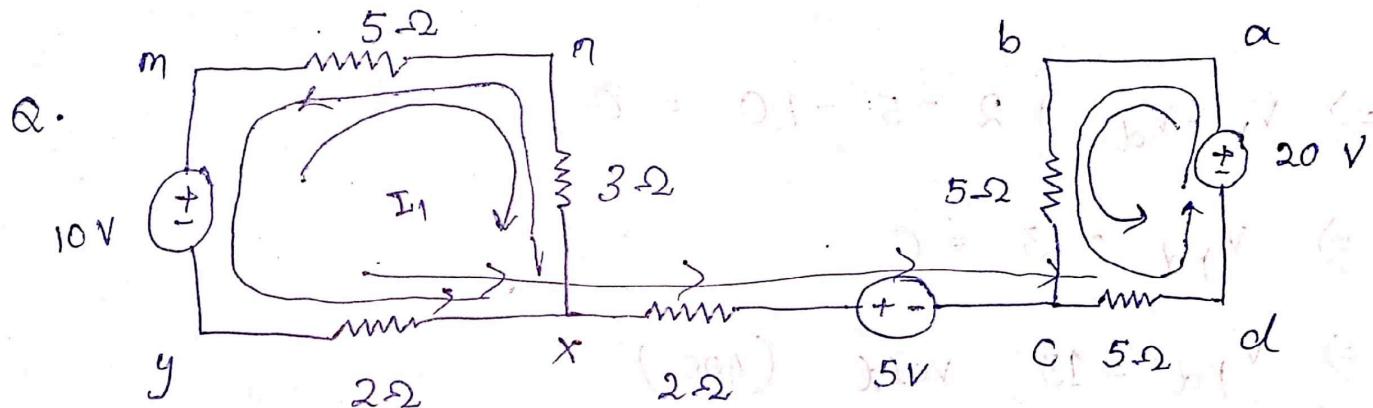
$$V_{ae} = -5 \text{ volt } (\underline{\text{Ans}})$$



Find the voltage drops bet' the terminal
y and d

Sol'

$$V_{yd} = V_y \pm V_{2\Omega} \pm V_{2\Omega} \pm 5V \pm V_{5\Omega} - V_d = 0$$

for loop ① ,

$$+3I_1 + 5I_1 - 10 + 2I_1 = 0$$

$$\Rightarrow 10I_1 = 10$$

$$\Rightarrow I_1 = 1 \text{ AMP}$$

for loop ②,

$$+20 - 5I_2 - 5I_2 = 0$$

$$\Rightarrow 20 - 10I_2 = 0$$

$$\Rightarrow 20 = 10I_2$$

$$\Rightarrow I_2 = 2 \text{ Amp}$$


$$V_Y + 2 \times 1 + 0 - 5 - 5 \times 2 - V_d = 0$$

$$\Rightarrow V_Y - V_d + 2 - 5 - 10 = 0$$

$$\Rightarrow V_Y - 13 = 0$$

$$\Rightarrow V_Y = 13 \text{ Volt (Ans.)}$$

Q -

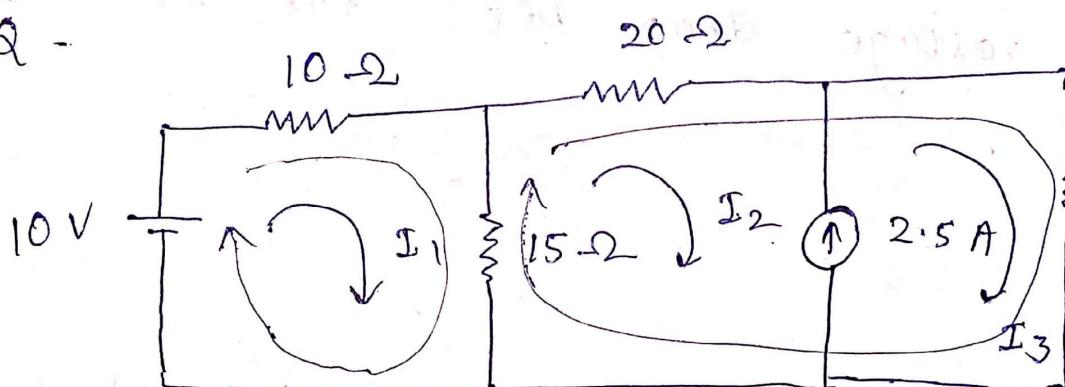

Find the current across 15Ω resistor using mesh analysis.

for loop ①,

$$10 - 10I_1 - 15(I_1 - I_2) = 0$$

$$\Rightarrow 10 - 10I_1 - 15I_1 + 15I_2 = 0$$

$$\Rightarrow 10 = 25I_1 - 15I_2 \quad \text{--- } ①$$

$$-20I_2 - 50I_3 - 15(I_2 - I_1) = 0$$

$$\Rightarrow -20I_2 - 50I_3 - 15I_2 + 15I_1 = 0$$

$$\Rightarrow 0 = 15I_1 - 35I_2 - 50I_3 \quad \text{--- } ②$$

$$I_2 - I_3 = -2.5$$

$$\Rightarrow I_3 - I_2 = 2.5$$

$$\Rightarrow 2.5 = I_3 - I_2$$

$$\Rightarrow 2.5 = -I_2 + I_3 \quad \text{--- } ③$$

$$\begin{bmatrix} 10 \\ 0 \\ 2.5 \end{bmatrix} = \begin{bmatrix} 25 & -15 & 0 \\ 15 & -35 & -50 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{1}{25} \begin{bmatrix} 10 & -15 & 0 \\ 0 & -35 & -50 \\ 2.5 & -1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 25 & -15 & 0 \\ 15 & -35 & -50 \\ 0 & -1 & 1 \end{bmatrix}$$

$$= \frac{10(-35 - 50) + 15(0 + 2.5)}{25(-35 - 50) + 15(15 + 0)}$$

$$= \frac{10(-85) + 15(125)}{25(-85) + 225}$$

$$= \frac{-850 + 1875}{-2125 + 225}$$

$$= \frac{1025}{-1900}$$

$$= -0.539 \text{ Amp}$$

$$I_2 = \frac{\begin{bmatrix} 25 & 10 & 0 \\ 15 & 0 & -50 \\ 0 & 2.5 & 1 \end{bmatrix}}{\begin{bmatrix} 25 & -15 & 0 \\ 15 & -35 & -50 \\ 0 & -1 & 1 \end{bmatrix}}$$

$$= \frac{25(0+125) - 10(15+0)}{-1900}$$

$$= \frac{3125 - 150}{-1900}$$


$$= \frac{2975}{-1900}$$

$$= -1.565 \text{ Amp}$$

$$I_1 - I_2 = -0.539 + 1.565$$

$$= 1.026 \text{ Amp}$$

Q.

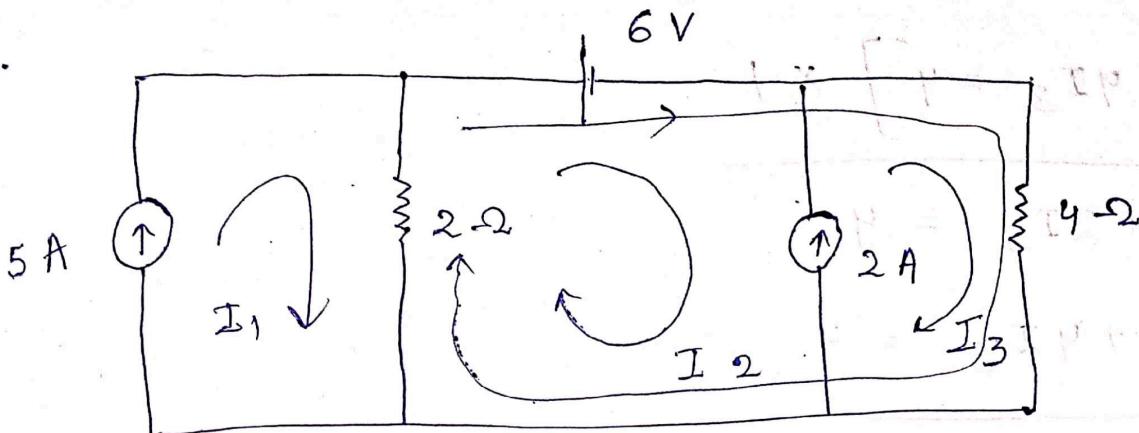

Find the current across 4 ohm resistor, using mesh analysis.

Sol'

$$-6 - 4I_3 - 2(I_2 - I_1) = 0$$

$$\Rightarrow -6 - 4I_3 - 2I_2 + 2I_1 = 0$$

$$\Rightarrow 2I_1 - 2I_2 - 4I_3 - 6 = 0 \quad \text{--- (1)}$$

$$I_1 = 5 \text{ A}$$

$$I_2 + 2 - I_3 = 0$$

$$2 = I_3 - I_2 \quad \text{--- (2)}$$

Put $I_1 = 5 \text{ A}$ in eqⁿ (1),

$$\Rightarrow 10 - 2I_2 - 4I_3 - 6 = 0$$

$$\Rightarrow -2I_2 - 4I_3 + 4 = 0$$

$$\Rightarrow -2I_2 - 4I_3 = -4$$

$$\Rightarrow 2I_2 + 4I_3 = 4 \quad \text{--- (3)}$$

$$[I_3 - I_2 = 2] \times 2$$

$$[2I_2 + 4I_3 = 4] \times 1$$

$$-2I_2 + 2I_3 = 4$$

$$2I_2 + 4I_3 = 4$$

$$6I_3 = 8$$

$$\Rightarrow I_3 = \frac{8}{6}$$


$$= 1.333 \text{ Amp} \quad (\text{Ans})$$

$$1.333 - I_2 = 2$$

$$\Rightarrow I_2 = 1.333 - 2$$

$$= -0.667 \text{ (Amp)}$$

Nodal Analysis :-

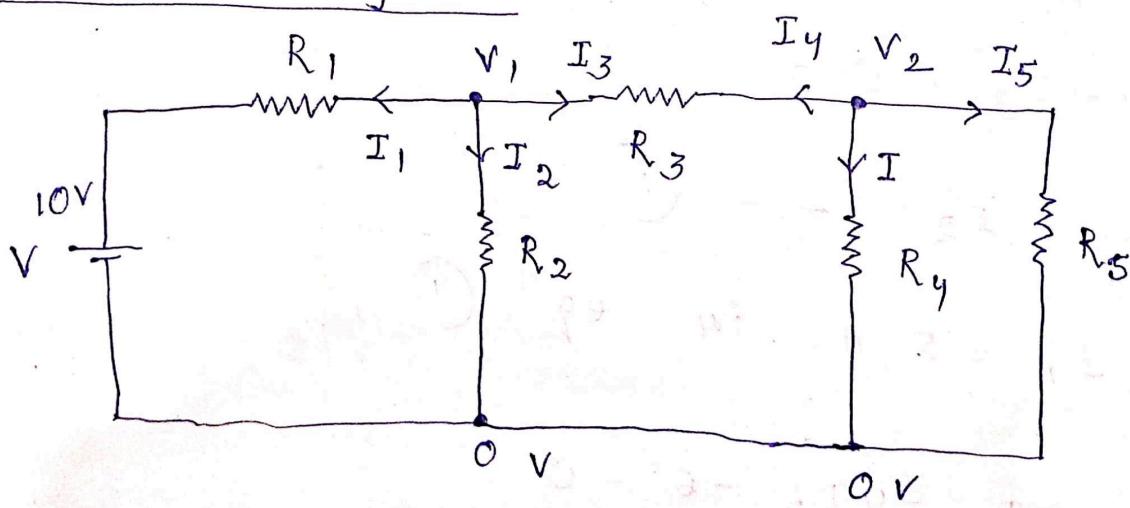


$$I_1 + I_2 + I_3 = 0$$

$$\therefore \frac{V_1 - 10}{R_1} + \frac{V_1 - 0}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$


$$I_4 + I + I_5 = 0$$
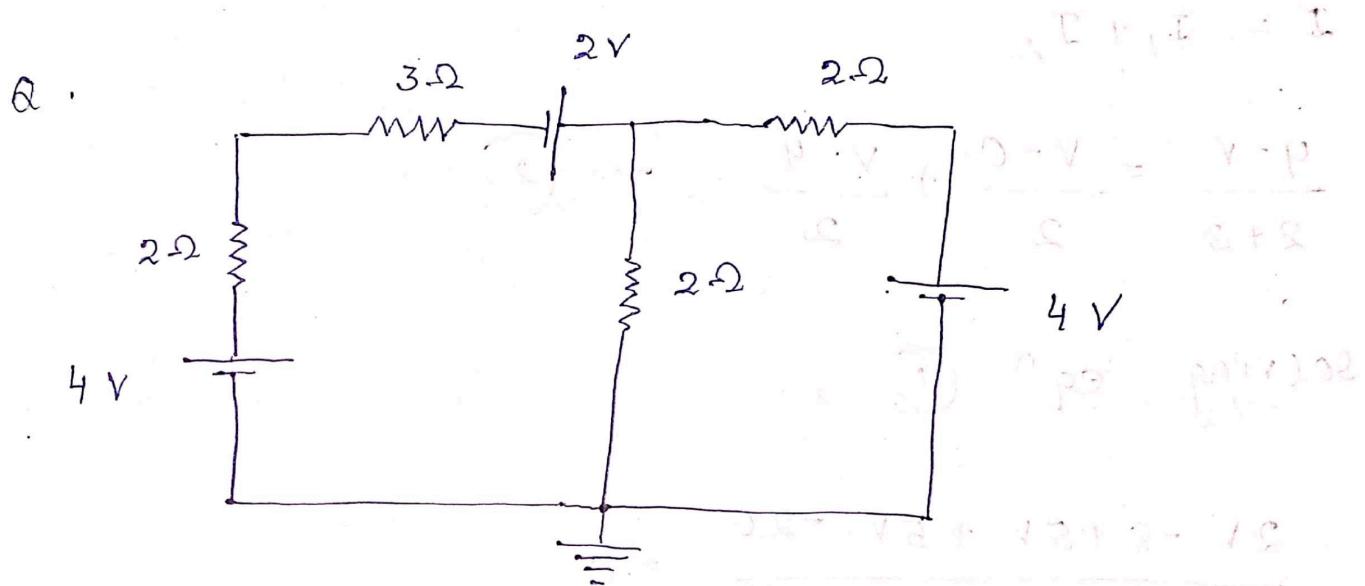
$$\therefore \frac{V_2 - V_1}{R_3} + \frac{V_2 - 0}{R_4} + \frac{V_2 - 0}{R_5} = 0$$




using nodal analysis find the current across
2Ω resistor.

Sol'

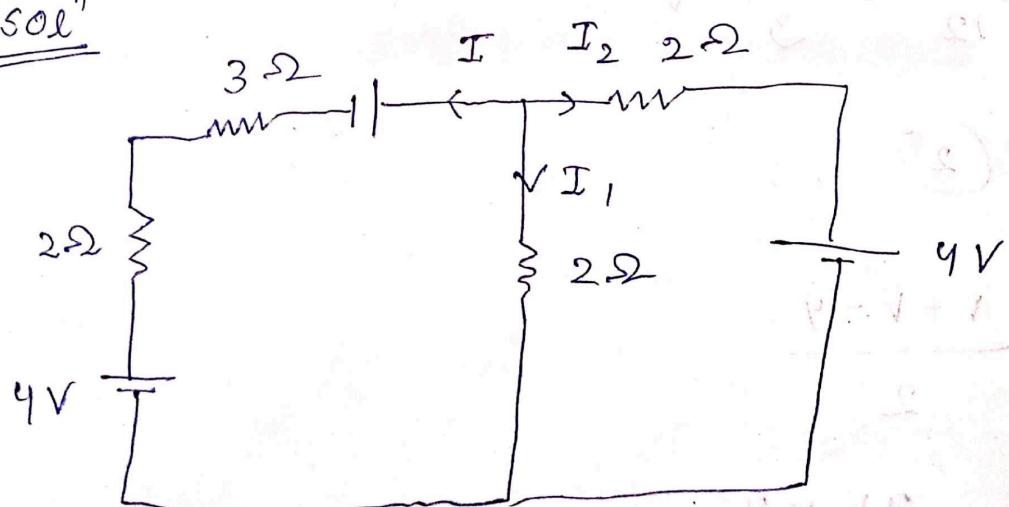

$$I + I_1 + I_2 = 0$$
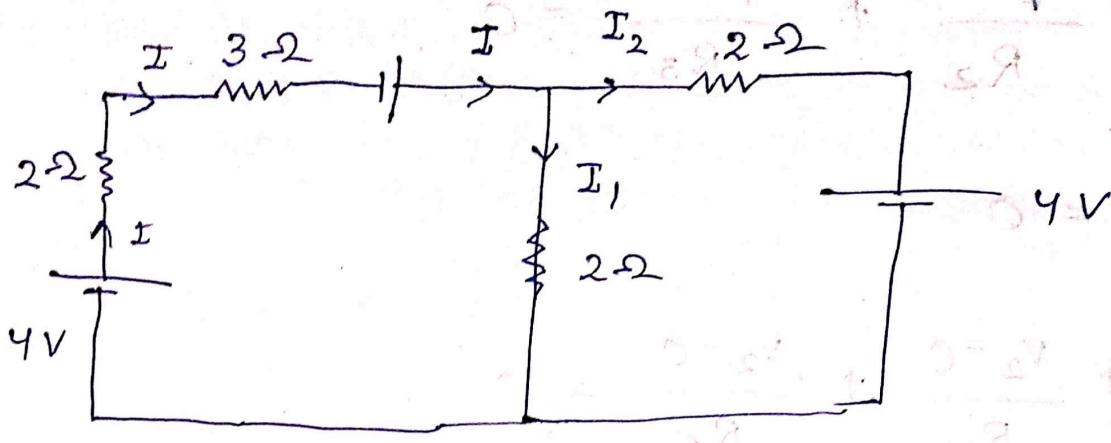
$$\frac{V-y}{2+3} + \frac{V-0}{2} + \frac{V-y}{2} = 0 \quad \text{--- (1)}$$



$$I = I_1 + I_2$$

$$\Rightarrow \frac{4-V}{2+3} = \frac{V-0}{2} + \frac{V-y}{2} \quad \text{--- (2)}$$

Solving eqⁿ (1),

$$\frac{2V - 8 + 5V + 5V - 20}{2+3} = 0$$

$$\Rightarrow 12V - 28 = 0$$

$$\Rightarrow V = \frac{28}{12} = \frac{7}{3} V$$

Solving eqⁿ (2),

$$\frac{4-V}{5} = \frac{V+V-y}{2}$$

$$\Rightarrow \frac{4-V}{5} = \frac{2V-y}{2}$$

$$\Rightarrow 8 - 2V = 10V - 20$$


$$\Rightarrow 12V = 28$$

$$\Rightarrow V = \frac{7}{3} \text{ volt}$$

$$I_1 = \frac{V}{2}$$

$$= \frac{\frac{7}{3}}{2}$$

$$= \frac{7}{6} \text{ Amp}$$

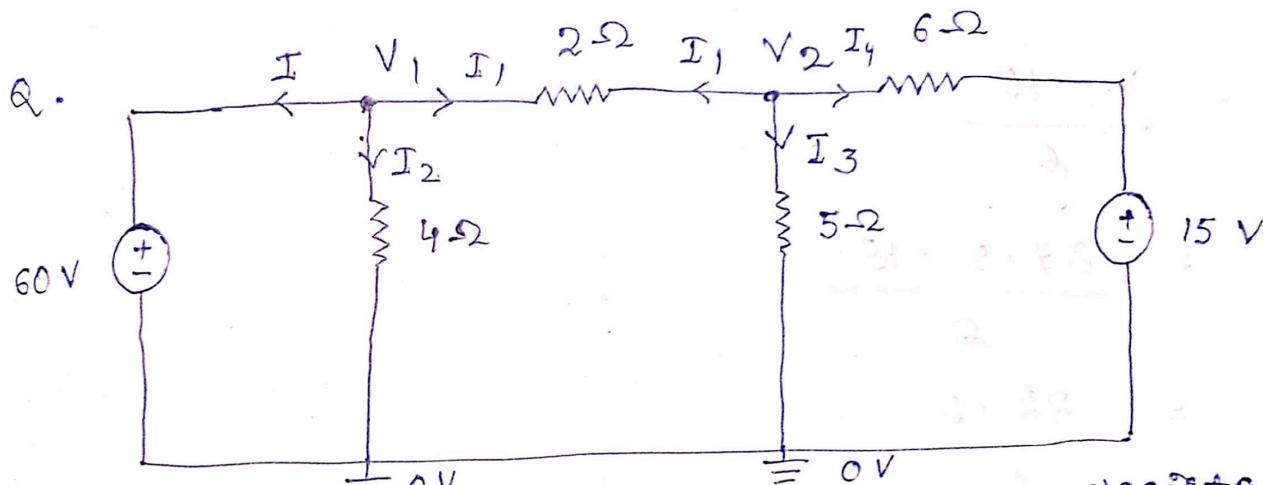

Find the current across 6Ω resistor.

Sol'

By applying KCL,
at node (1),

$$V_1 = 60$$

at node (2),

$$I_1 + I_3 + I_4 = 0$$

$$\Rightarrow \frac{V_2 - V_1}{2} + \frac{V_2 - 0}{5} + \frac{V_2 - 15}{6} = 0$$

$$\Rightarrow \frac{15V_2 - 900 + 6V_2 + 5V_2 - 75}{30} = 0$$

$$\Rightarrow 26V_2 - 975 = 0$$

$$\Rightarrow 26V_2 = 975$$

$$\Rightarrow V_2 = \frac{975}{26}$$

$$= 37.5 \text{ V}$$


$$I_4 = \frac{V_2 - 15}{6}$$

$$= \frac{37.5 - 15}{6}$$

$$= \frac{22.5}{6}$$

$$= 3.75 \text{ Amp}$$

Q.

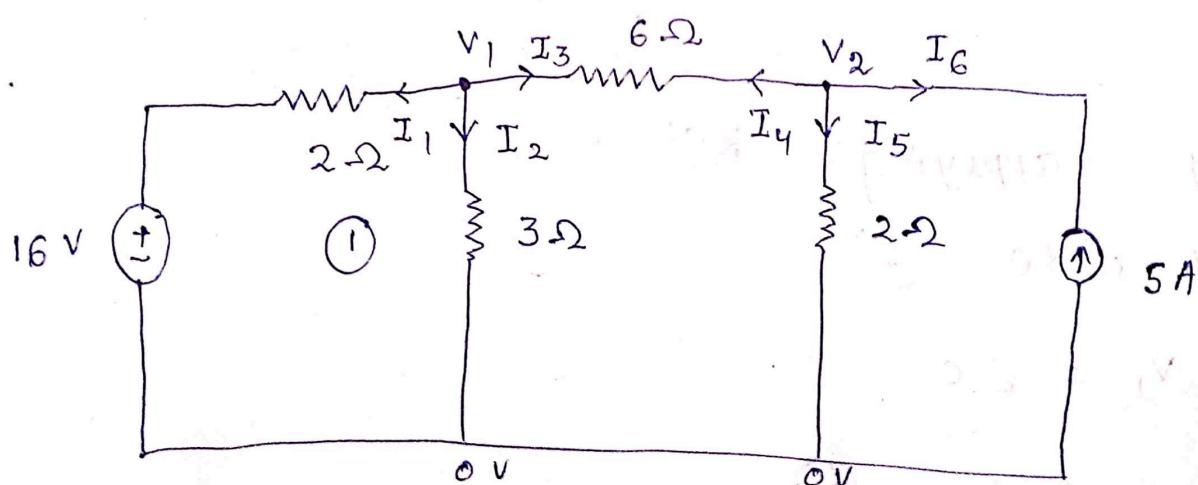

using nodal analysis find the current across 2Ω resistor.

Applying KCL for node ①,

$$I_1 + I_2 + I_3 = 0 \quad \text{--- (1)}$$

$$\Rightarrow \frac{v_1 - 16}{2} + \frac{v_1 - 0}{3} + \frac{v_1 - v_2}{6} = 0 \quad \text{--- (1)}$$

applying KCL at node ②;

$$I_4 + I_5 + I_6 = 0$$

$$\Rightarrow \frac{v_2 - v_1}{6} + \frac{v_2 - 0}{2} + (-5) = 0 \quad \text{--- (2)}$$

solving eq ①,

$$\Rightarrow \frac{3v_1 - 48 + 2v_1 + v_1 - v_2}{6} = 0$$

$$\Rightarrow 6v_1 - v_2 - 48 = 0$$

$$\Rightarrow 6v_1 - v_2 = 48 \quad \text{--- (3)}$$

solving eq ②,

$$\Rightarrow \frac{v_2 - v_1 + 3v_2 - 30}{6} = 0$$

$$\Rightarrow 4v_2 - v_1 - 30 = 0$$

$$\Rightarrow -v_1 + 4v_2 = 30 \quad \text{--- (4)}$$

$$\text{eq}^7 \quad (3) \times 1 \Rightarrow 6V_1 - V_2 = 48$$

$$\text{eq}^7 \quad (4) \times 6 \Rightarrow -6V_1 + 24V_2 = 180$$

$$23V_2 = -228$$

$$\Rightarrow V_2 = \frac{-228}{23}$$

$$= 9.913 \text{ volt}$$

putting the value of V_2 in eq⁷ (3),

$$6V_1 - V_2 = 48$$

$$\Rightarrow 6V_1 - 9.913 = 48$$

$$\Rightarrow 6V_1 = 57.913$$


$$\Rightarrow V_1 = 9.652 \text{ volt}$$

$$I_1 = \frac{V_1 - 16}{2}$$

$$= \frac{9.652 - 16}{2}$$

$$= -3.174 \text{ AMP}$$

$$= 3.174 \text{ AMP}$$

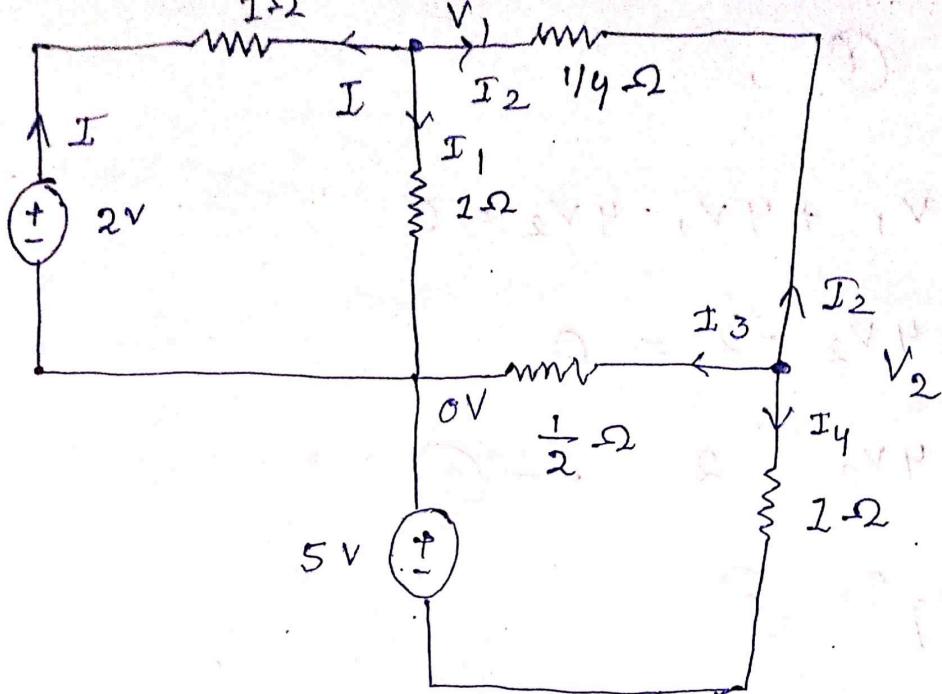

using nodal analysis find the current through 2V source.

Sol'

Applying KCL at node - 1,

$$I + I_1 + I_2 = 0$$

$$\Rightarrow \frac{V_1 - 2}{1} + \frac{V_1 - 0}{1} + \frac{V_1 - V_2}{1/4} = 0 \quad \text{--- (1)}$$

Applying KCL at node - 2,

$$I_2 + I_3 + I_4 = 0$$

$$\Rightarrow \frac{V_2 - V_1}{1/4} + \frac{V_2 - 0}{1/2} + \frac{V_2 + 5}{1} = 0 \quad \text{--- (2)}$$

Solving eqⁿ ①,

$$\Rightarrow v_1 - 2 + v_1 + 4v_1 - 4v_2 = 0$$

$$\Rightarrow 6v_1 - 4v_2 - 2 = 0 \dots$$

$$\Rightarrow 6v_1 - 4v_2 = 2 \rightarrow \textcircled{3}$$

Solving eqⁿ ②

$$4v_2 - 4v_1 + 2v_2 + v_2 + 5 = 0$$

$$\Rightarrow -4v_1 + 7v_2 = -5 \rightarrow \textcircled{4}$$

Multiply 4 x eqⁿ ③

Multiply 6 x eqⁿ ④

$$\Rightarrow 24v_1 - 16v_2 = 8$$

$$\Rightarrow -24v_1 + 42v_2 = -30$$

$$26v_2 = -22$$

$$\Rightarrow v_2 = -0.846 \text{ volt}$$

$$6v_1 - 4(-0.846) = 2$$

$$\Rightarrow 6v_1 + 3.384 = 2$$

$$\Rightarrow 6v_1 = 2 - 3.384$$


$$\Rightarrow 6v_1 = -1.384$$

$$\Rightarrow v_1 = -0.23 \text{ volt}$$


$$I = \frac{\frac{V_1 - 2}{1}}{1}$$

$$= \frac{-0.23 - 2}{1}$$

$$= -2.23 \text{ Amp}$$

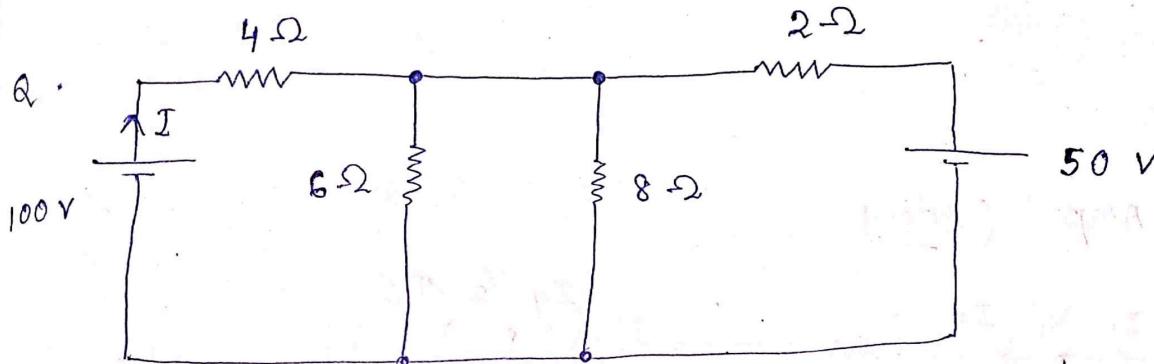

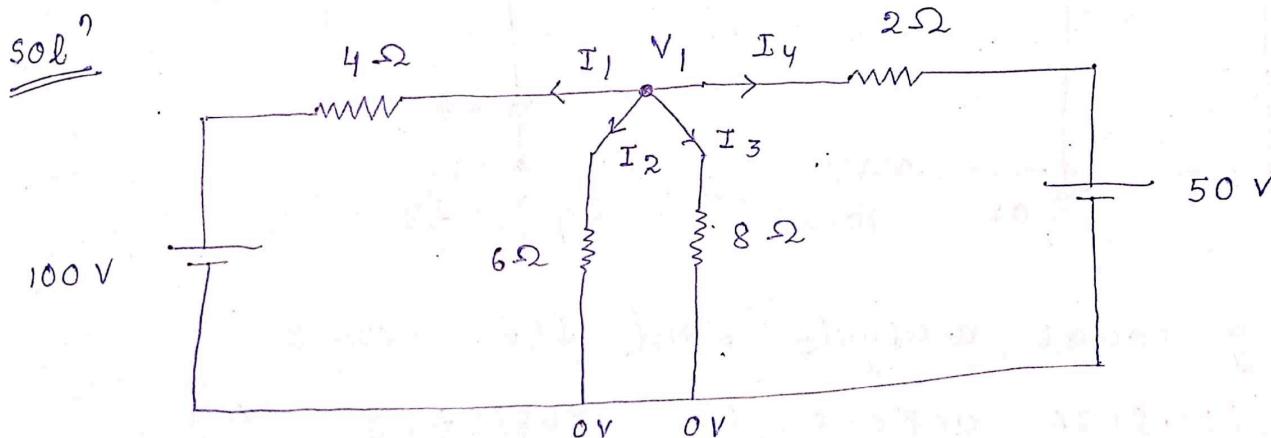using nodal analysis find the current through 6Ω resistor.



Applying KCL at node 1,

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\Rightarrow \frac{V_1 - 100}{4} + \frac{V_1 - 0}{6} + \frac{V_1 - 0}{8} + \frac{V_1 - 50}{2} = 0$$

$$\Rightarrow \frac{6V_1 - 600 + 4V_1 + 3V_1 + 12V_1 - 600}{24} = 0$$

$$\Rightarrow 25V_1 = 1200$$

$$\Rightarrow V_1 = \frac{1200}{25}$$


$$= 48 \text{ volt}$$

$$I_2 = \frac{V_1}{6}$$

$$= \frac{48}{6}$$

$$= 8 \text{ Amp } (\underline{\text{Ans}})$$

Q.

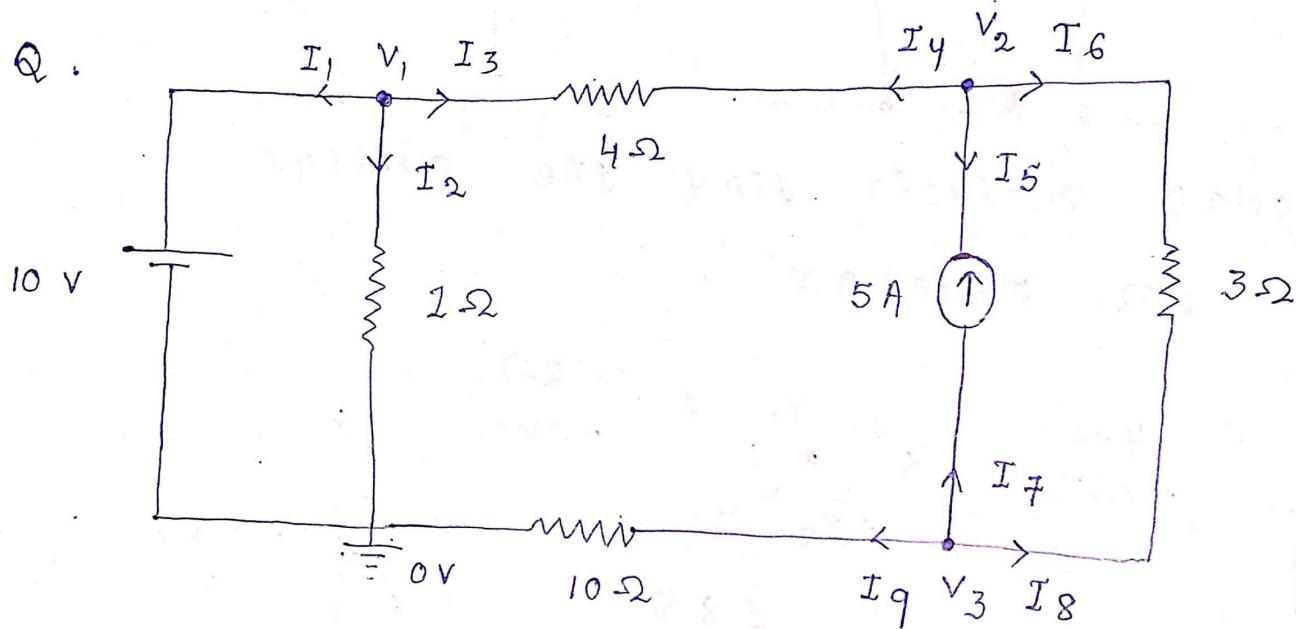

Using nodal analysis find the power dissipation across 4Ω resistor and current at 10Ω resistor.

Soln

Applying KCL at node ①,

$$I_1 + I_2 + I_3 = 0$$

$$V_1 - 0 = 10$$

$$\Rightarrow V_1 = 10 \text{ volt}$$

Applying KCL at node ②,

$$I_4 + I_5 + I_6 = 0$$

$$\Rightarrow \frac{V_2 - V_1}{4} + (-5) + \frac{V_2 - 0}{3} = 0$$

$$\Rightarrow \frac{V_2 - V_1}{4} - 5 + \frac{V_2 - V_3}{3} = 0$$

~~$$\Rightarrow \frac{3V_2 - 3V_1}{12} - 60 + 4V_2 = 0$$~~

~~$$\Rightarrow 7V_2$$~~

$$\Rightarrow \frac{3V_2 - 3V_1 - 60 + 4V_2 - 4V_3}{12} = 0$$

$$\Rightarrow -3V_1 + 7V_2 - 4V_3 = 60$$

$$\Rightarrow -30 + 7V_2 - 4V_3 = 60$$

$$\Rightarrow 7V_2 - 4V_3 = 90 \quad - ①$$

Applying KCL at node ③

$$I_7 + I_8 + I_9 = 0$$

$$\Rightarrow 5 + \frac{V_3 - V_2}{3} + \frac{V_3 - 0}{10} = 0$$

$$\Rightarrow \frac{150 + 10V_3 - 10V_2 + 3V_3}{30} = 0$$

$$\Rightarrow -10V_2 + 13V_3 = -150 \quad \text{--- (2)}$$

$$\text{eq } ① \times 10 \Rightarrow 70V_2 - 40V_3 = 900$$

$$\text{eq } ② \times 7 \Rightarrow -70V_2 + 91V_3 = -1050$$
$$\underline{51V_3 = -150}$$

$$\Rightarrow V_3 = \frac{-150}{51}$$

$$= -2.941 \text{ volt}$$

Putting the value of V_3 in eq ②,

$$\Rightarrow -10V_2 + 13(-2.941) = -150$$


$$\Rightarrow -10V_2 - 38.233 = -150$$

$$\Rightarrow -10V_2 = -150 + 38.233$$

$$\Rightarrow -10V_2 = -111.767$$

$$\Rightarrow V_2 = 11.176 \text{ volt}$$

super node Analysis :-

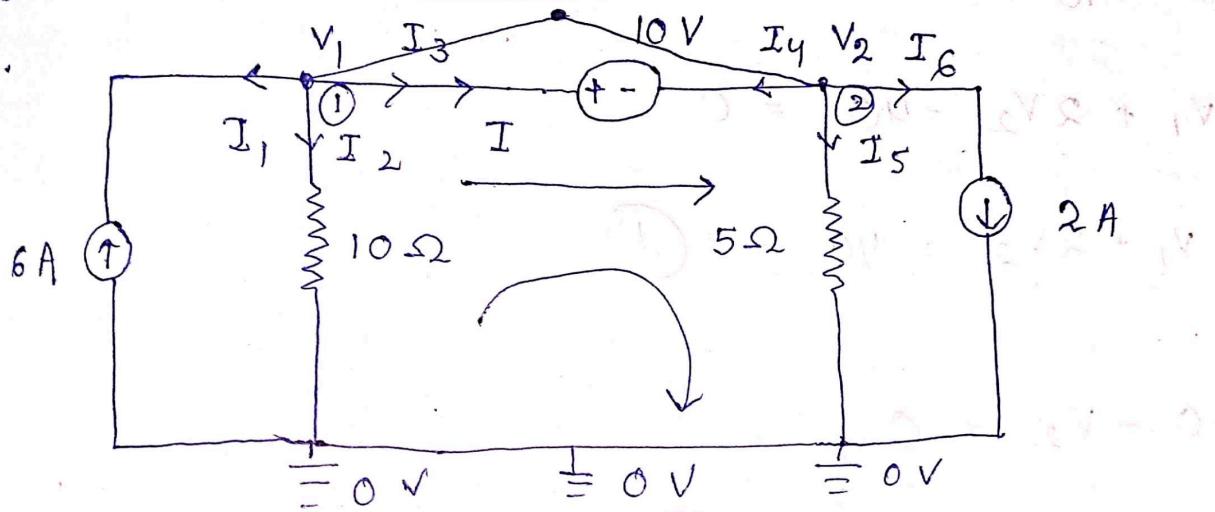

using super node analysis find the current

I.

Sol

Applying KCL at node ①,

$$I_1 + I_2 + I_3 = 0$$

$$\Rightarrow -6 + \frac{V_1 - 0}{10} + I_3 = 0$$

Applying KCL at node ②,

$$I_4 + I_5 + I_6 = 0$$

$$\Rightarrow I_4 + \frac{V_2 - 0}{5} + 2 = 0$$

$$I_1 + I_2 + I_5 + I_6 = 0$$

$$-6 + \frac{V_1}{10} + \frac{V_2}{5} + 2 = 0$$

$$\Rightarrow \frac{-60 + V_1 + 2V_2 + 20}{10} = 0$$

$$\Rightarrow V_1 + 2V_2 - 40 = 0$$

$$\Rightarrow V_1 + 2V_2 = 40 \quad \text{--- (1)}$$

$$V_1 - 10 - V_2 = 0$$

$$\Rightarrow V_1 - V_2 = 10 \quad \text{--- (2)}$$

Subtracting eqⁿ (2) from eqⁿ (1),

$$2V_2 + V_2 = 30$$


$$\Rightarrow 3V_2 = 30$$

$$\Rightarrow V_2 = 10 \text{ volt}$$

Putting the value of V_2 in eqⁿ (2),

$$V_1 - 10 = 10$$
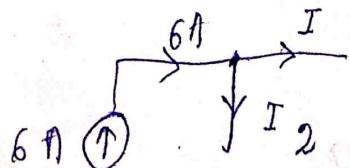
$$\Rightarrow V_1 = 20 \text{ volt} \quad (\text{Ans})$$



$$6 = I_2 + I$$

$$\Rightarrow 6 = \frac{V_1}{10} + I$$

$$\Rightarrow 6 = \frac{20}{10} + I$$

$$\Rightarrow 6 = 2 + I$$


$$\Rightarrow I = 4 \text{ Amp (Ans)}$$

Q.

$$I_4 + I_5 + I_6 = 0$$

$$\Rightarrow I_4 + 2 + 2 = 0$$
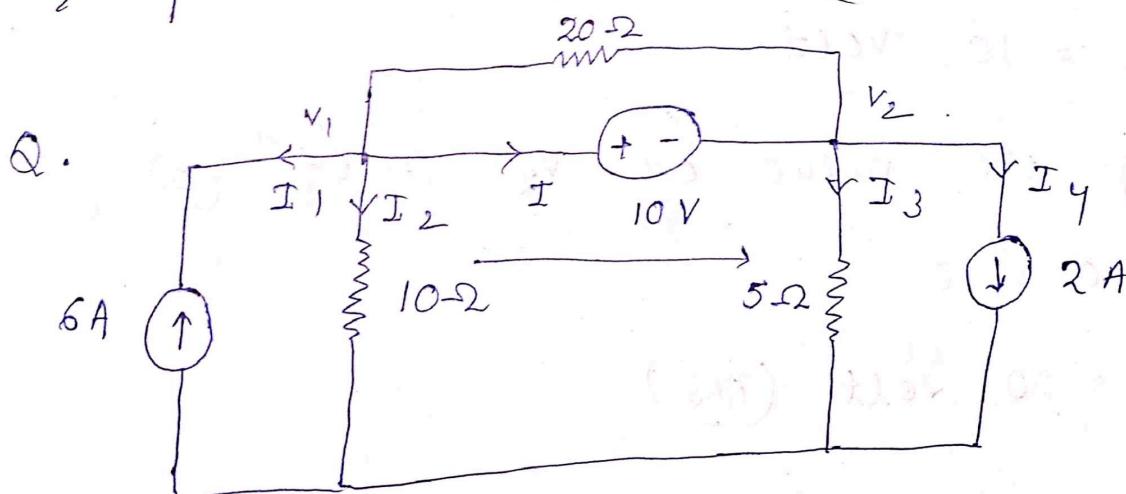
$$\Rightarrow I_4 = -4 \text{ Amp (Ans)} \quad (\because \text{opposite direction})$$



using supernode analysis find the current

I.

$$\text{sol}^n \quad I_1 + I_2 + I_3 + I_4 = 0$$

$$-6 + \frac{V_1}{10} + \frac{V_2}{5} + 2 = 0$$

$$\Rightarrow \frac{-60 + V_1 + 2V_2 + 20}{10} = 0$$

$$\Rightarrow V_1 + 2V_2 - 40 = 0$$

$$\Rightarrow V_1 + 2V_2 = 40 \quad \text{--- (1)}$$

$$V_1 - 10 - V_2 = 0$$

$$\Rightarrow V_1 - V_2 = 10 \quad \text{--- (2)}$$

Subtracting eqⁿ (2) from eqⁿ (1),

$$2V_2 + V_2 = 30$$


$$\Rightarrow 3V_2 = 30$$

$$\Rightarrow V_2 = 10 \text{ volt}$$

Putting the value of V_2 in eqⁿ (2),

$$V_1 - 10 = 10$$
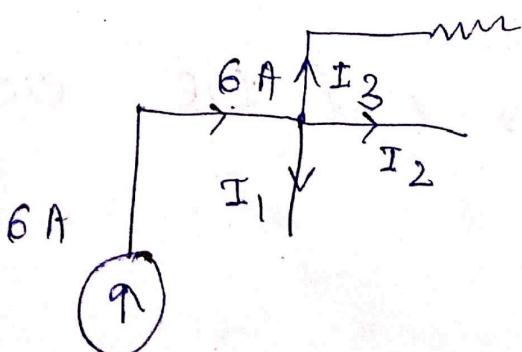
$$\Rightarrow V_1 = 20 \text{ volt (Ans)}$$




$$6 = I_1 + I_2 + I_3$$

$$\Rightarrow 6 = \frac{V_1}{10} + I_2 + \frac{V_1 - V_2}{20}$$

$$\Rightarrow 6 = \frac{20}{10} + I_2 + \frac{20 - 10}{20}$$

$$\Rightarrow 6 = 2 + I_2 + 0.5$$
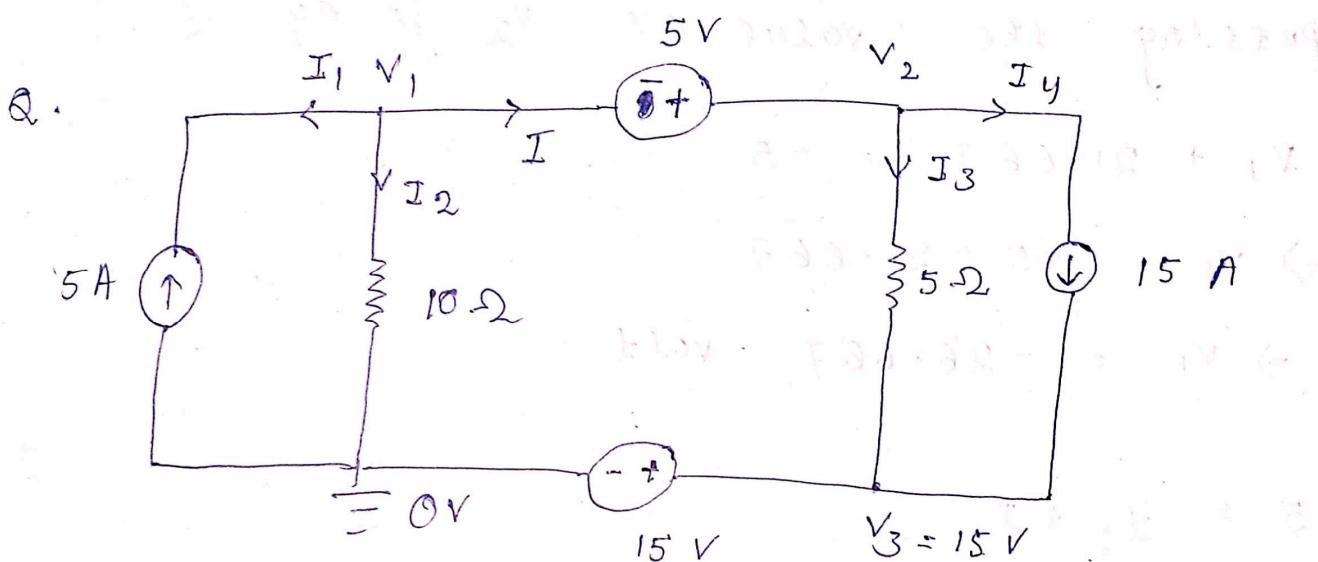
$$\Rightarrow I_2 = 3.5 \text{ Amp} \quad (\text{Ans})$$



using nodal analysis find the current 'I'.

Sol'

$$I_1 + I_2 + I_3 + I_y = 0$$

$$\Rightarrow -5 + \frac{V_1}{10} + \frac{V_2 - V_3}{5} + 15 = 0$$

$$\Rightarrow -5 + \frac{V_1}{10} + \frac{V_2 - 15}{5} + 15 = 0$$

$$\Rightarrow \frac{V_1}{10} + \frac{V_2 - 15}{5} = -10$$

$$\Rightarrow V_1 + 2V_2 - 30 = -100$$

$$\Rightarrow V_1 + 2V_2 = -70 \quad \text{--- (1)}$$

$$V_1 + 5 - V_2 = 0$$

$$\Rightarrow V_1 - V_2 = -5 \quad \text{--- (2)}$$

Subtracting eq' (2) from eq' (1),

$$2V_2 + V_2 = -65$$

$$\Rightarrow 3V_2 = -65$$

$$\Rightarrow V_2 = -21.667 \text{ volt}$$

Putting the value of V_2 in eq' (2),

$$V_1 + 21.667 = -5$$

$$\Rightarrow V_1 = -5 - 21.667$$

$$\Rightarrow V_1 = -26.667 \text{ volt}$$

$$5 = I_2 + I$$




$$\Rightarrow 5 = \frac{V_1}{10} + I$$

$$\Rightarrow 5 = \frac{-26.667}{10} + I$$

$$\Rightarrow I = 5 + 2.6667$$


$$\Rightarrow I = 7.6667 \text{ amp } (\underline{\text{Ans}})$$

source conversion technique :-

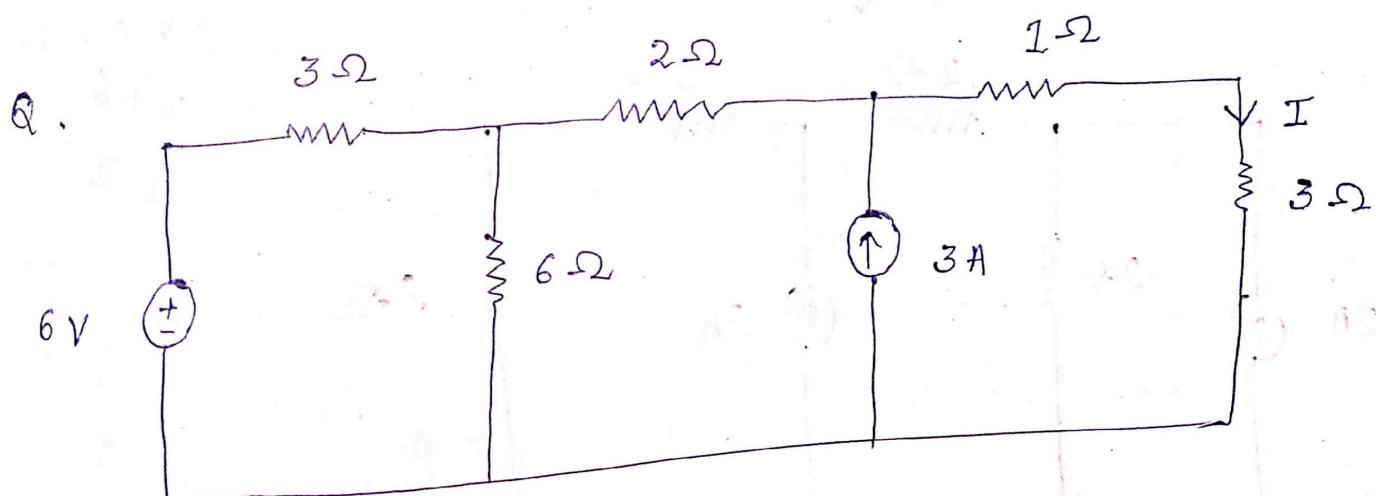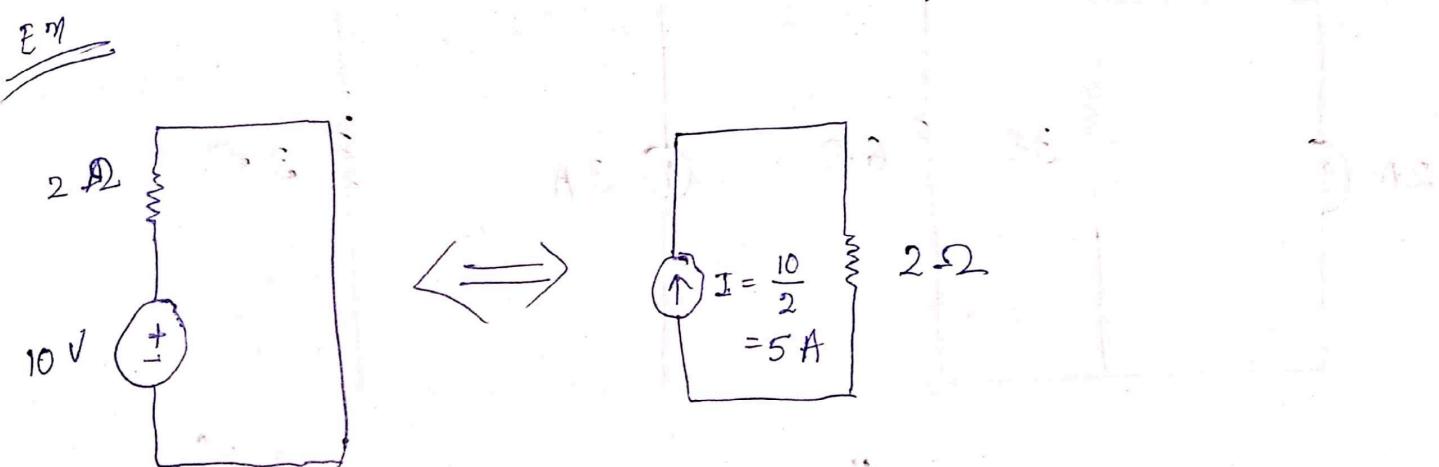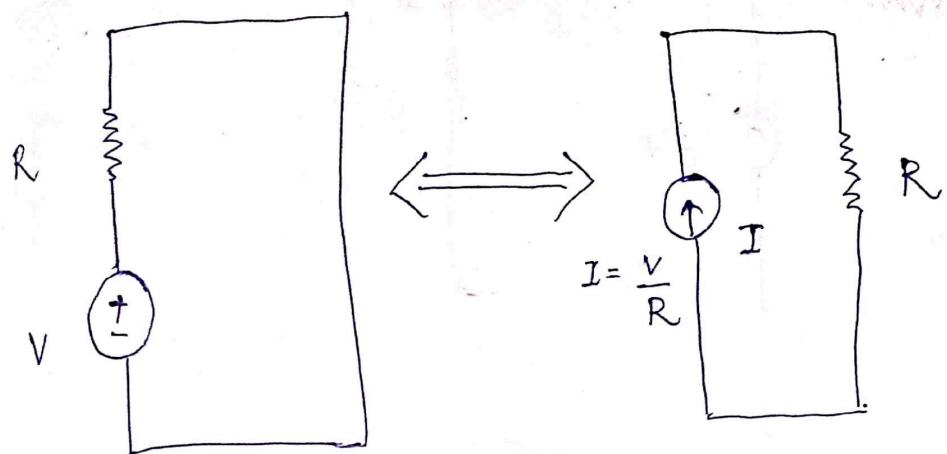


using source conversion technique find
the current I

Sol'

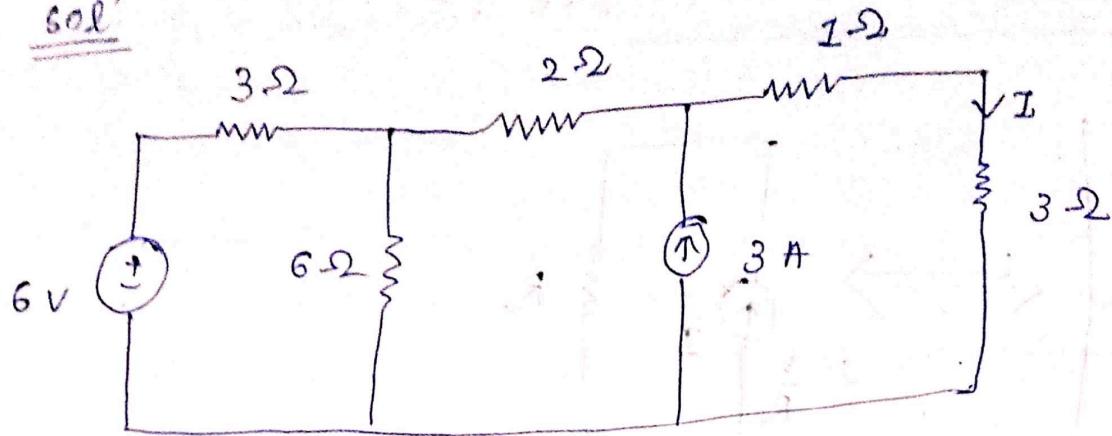


↓

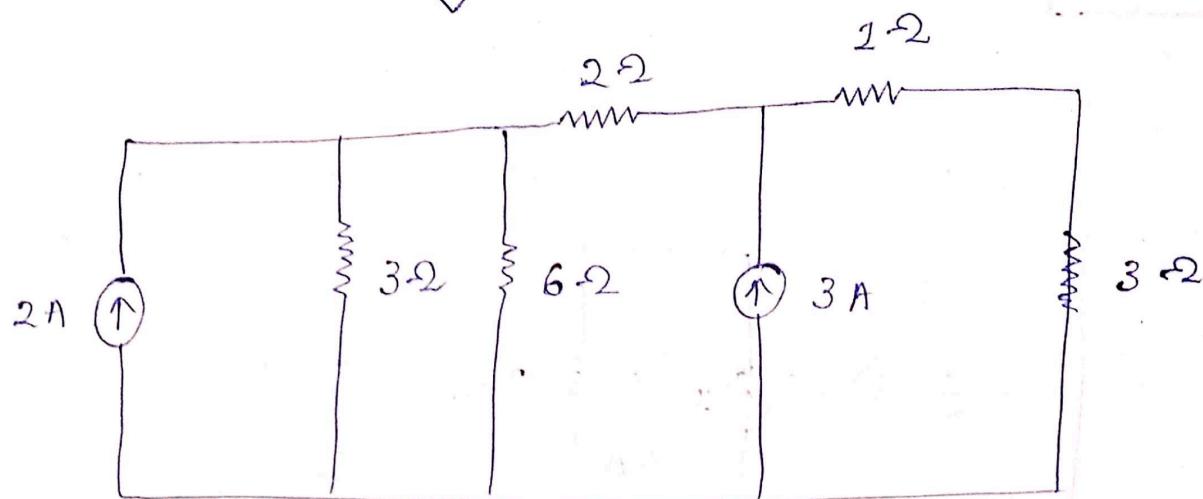


3 II 6


$$= \frac{3 \times 6}{3 + 6}$$

$$= 2 \Omega$$

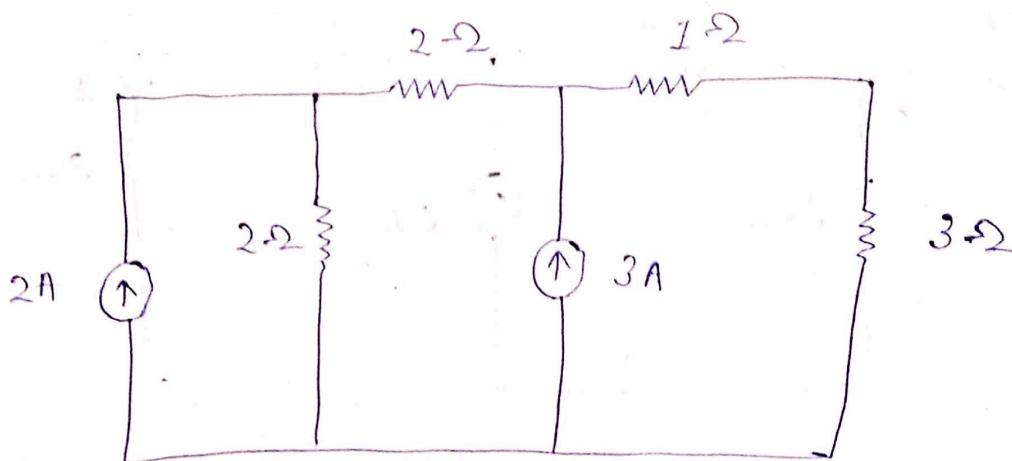


↓

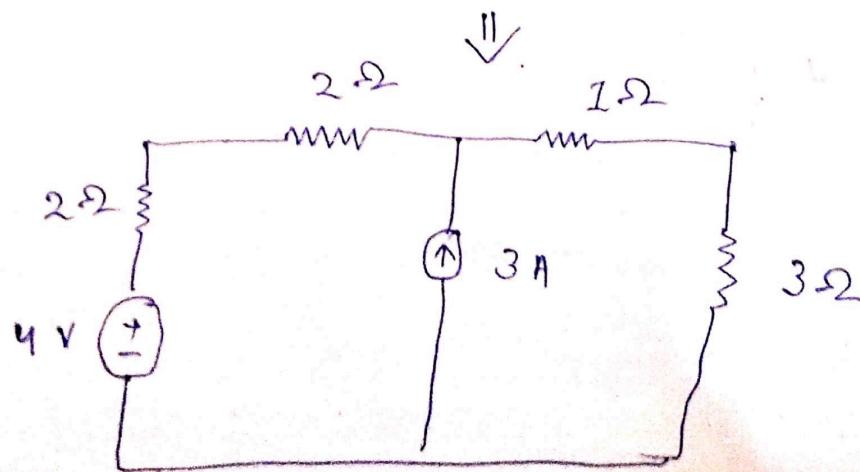


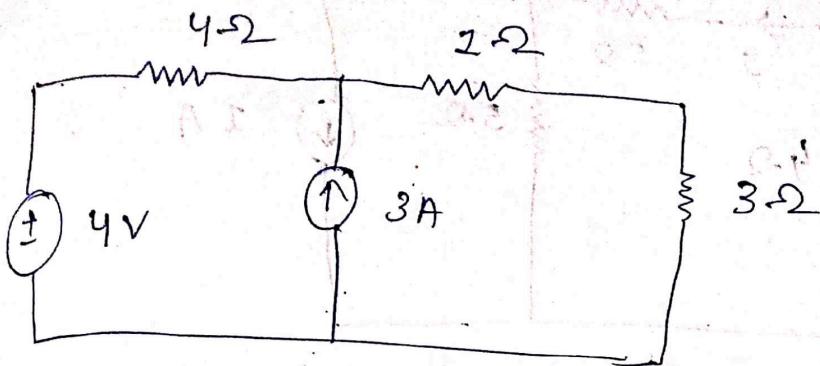


↓

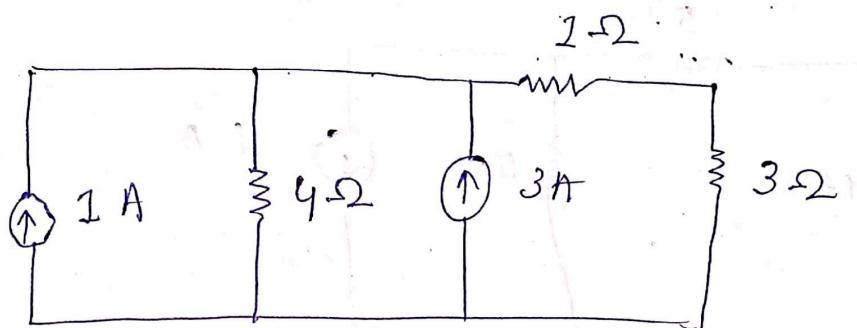

↓

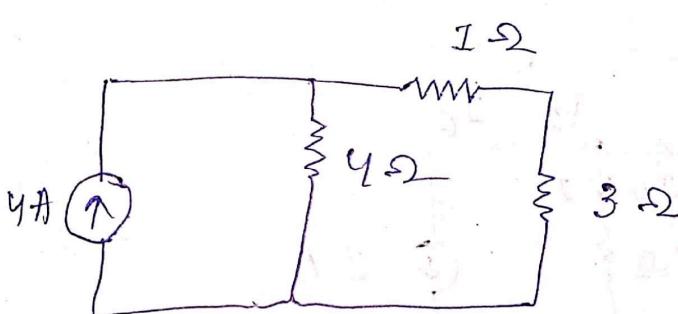

↓

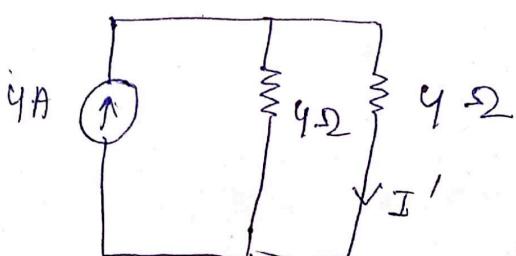


$$I + 3 = 4A$$



$$I' = \frac{I \times 4}{4 + 4}$$

$$= \frac{4 \times 4}{4 + 4}$$

$$= 2 \text{ AMP}$$

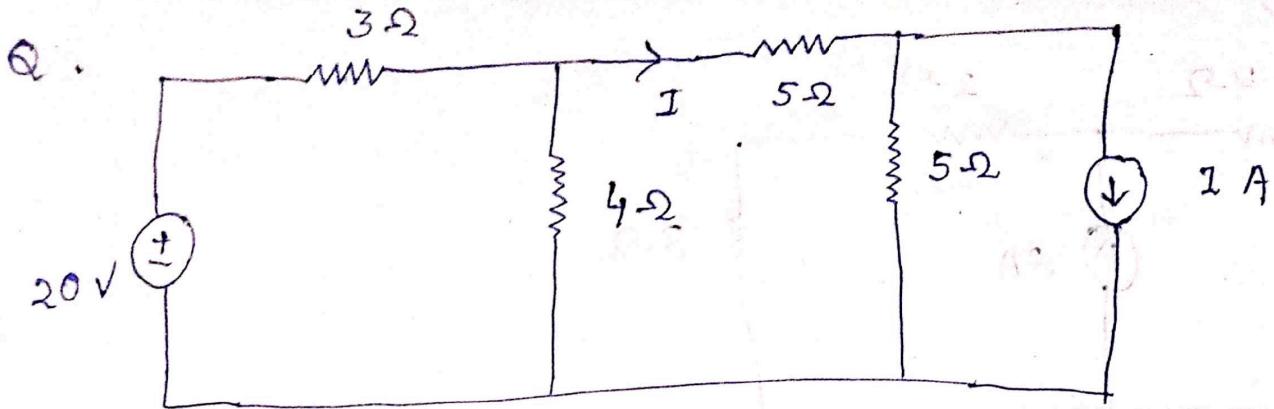

sol?

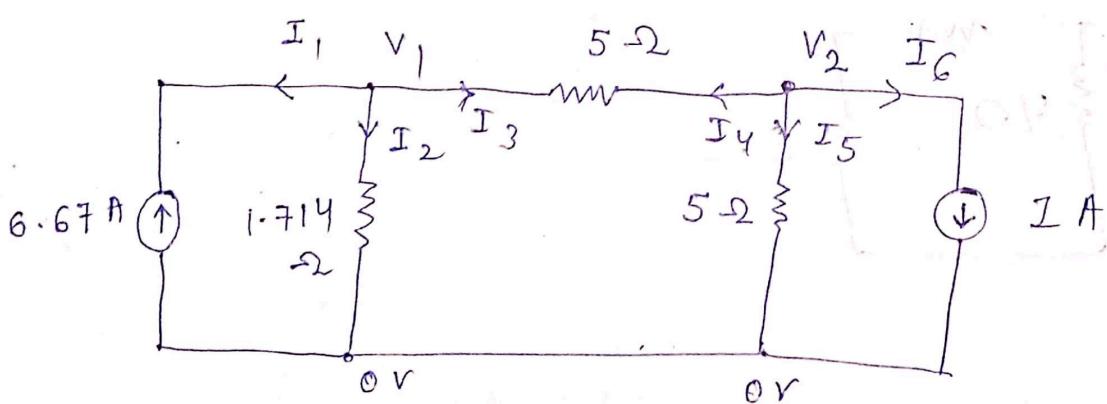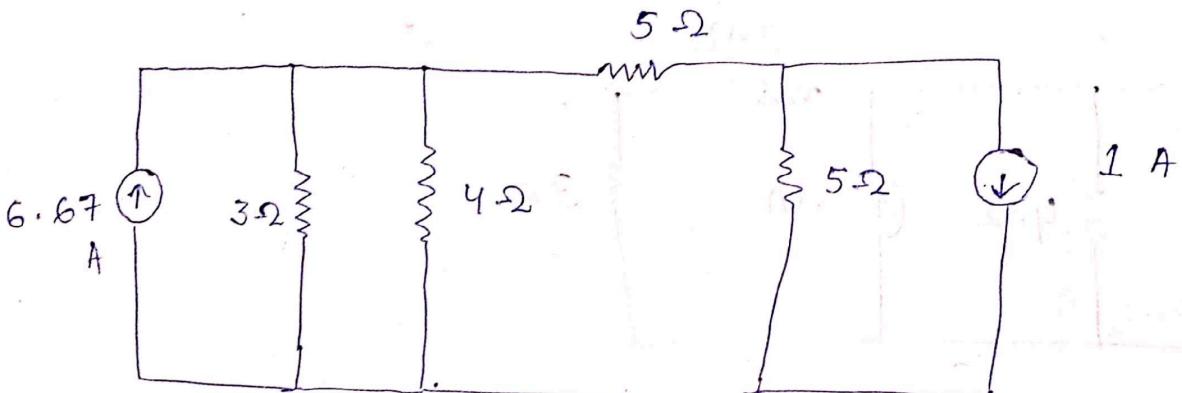

for node ①,

$$I_1 + I_2 + I_3 = 0$$

$$\Rightarrow -6.67 + \frac{V_1}{1.714} + \frac{V_1 - V_2}{5} = 0$$

$$\Rightarrow \frac{-57.161 + 5V_1 + 1.714V_1 - 1.714V_2}{8.57} = 0$$

$$6 \cdot 714 v_1 - 1 \cdot 714 v_2 = 57 \cdot 161 \quad \text{--- (1)}$$

for node (2),

$$I_4 + I_5 + I_6 = 0$$

$$\Rightarrow \frac{v_2 - v_1}{5} + \frac{v_2}{5} + 1 = 0$$

$$\Rightarrow \frac{v_2 - v_1 + v_2 + 5}{5} = 0$$

$$\Rightarrow -v_1 + 2v_2 = -5$$

$$\Rightarrow v_1 - 2v_2 = 5 \quad \text{--- (2)}$$

$$\text{Eq } (1) \times 1 \Rightarrow 6 \cdot 714 v_1 - 1 \cdot 714 v_2 = 57 \cdot 161$$

$$\text{Eq } (2) \times 6 \cdot 714 \Rightarrow \underline{\underline{6 \cdot 714 v_1 - 13 \cdot 428 v_2 = 33 \cdot 57}}$$

$$\Rightarrow 11 \cdot 714 v_2 = 23 \cdot 591$$

$$\Rightarrow v_2 = 2.013 \text{ volt}$$

$$v_1 = 9.026 \text{ volt}$$



$$\Rightarrow v_1 = 9.026 \text{ volt} \quad (\underline{\text{Ans}})$$

$$I = \frac{v_1 - v_2}{5}$$

$$= \frac{9.026 - 2.013}{5}$$

$$= 1.402 \text{ Amp} \quad (\underline{\text{Ans}})$$

Delta / star Transformation :-

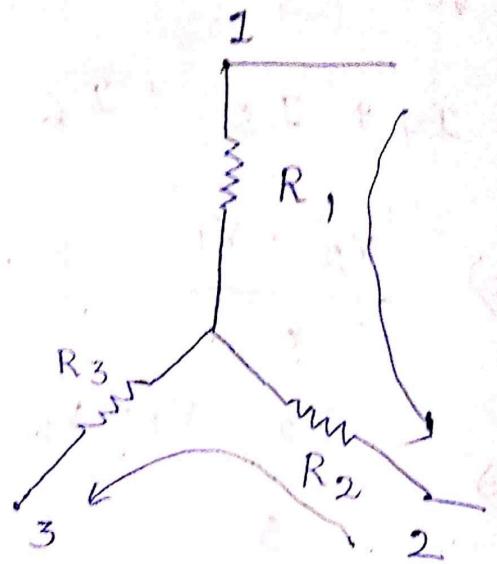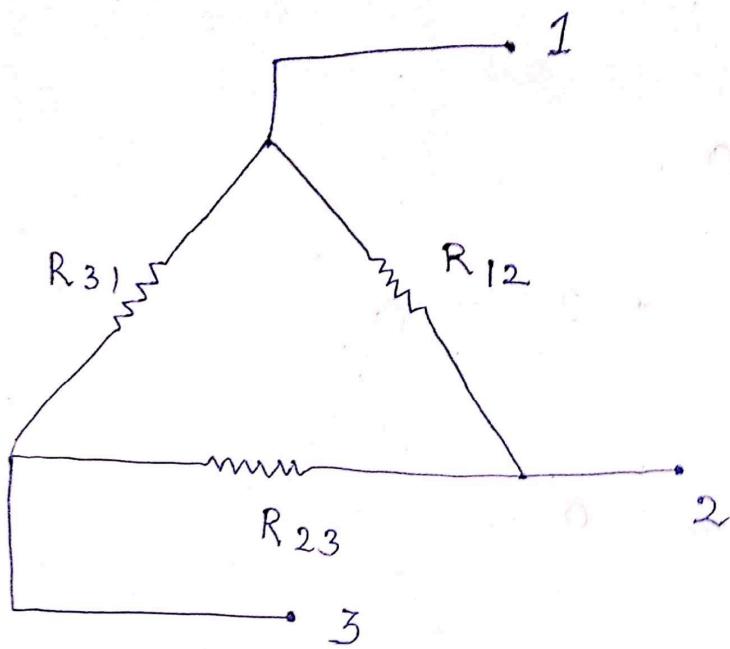

$$R_{12} = \frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

$$R_{12} = R_1 + R_2$$

$$\frac{R_{12} \times (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} = R_1 + R_2 \quad \textcircled{1}$$

$$R_{23} = R_{23} // (R_{12} + R_{31}) \quad R_{23} = R_2 + R_3$$

$$\Rightarrow R_{23} = \frac{R_{23} \times (R_{12} + R_{31})}{R_{23} + R_{12} + R_{31}}$$

$$R_{23} = R_2 + R_3 = \frac{R_{23} \times (R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \textcircled{2}$$

$$R_{31} = R_{31} \times (R_{12} + R_{23})$$

$$= \frac{R_{31} \times (R_{12} + R_{23})}{R_{31} + R_{12} + R_{23}}$$

$$R_{31} = \frac{R_{31} \times (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} = R_3 + R_1 \quad \text{--- (3)}$$

Subtracting eqⁿ (2) from eqⁿ (1),

$$R_1 + R_2 - (R_2 + R_3) = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} - \frac{R_{23} (R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow R_1 - R_2 - R_3 = \frac{R_{12} R_{23} + R_{12} R_{31} - R_{23} R_{12} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow R_1 - R_3 = \frac{R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (4)}$$

Adding eqⁿ (3) and eqⁿ (4),

$$R_1 + R_3 = \frac{R_{31} R_{12} + R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} \quad \text{--- (3)}$$

Adding eqⁿ ③ and eqⁿ ④ ,

$$R_1 + R_3 + R_1 - R_3 = \frac{R_{31} R_{12} + R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} + \frac{R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow 2R_1 = \frac{R_{31} R_{12} + R_{31} R_{23} + R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow 2R_1 = \frac{2 R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\Rightarrow R_1 = \boxed{\frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}}$$

$$\boxed{R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}}$$

$$\boxed{R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}}$$


star / delta transformation :-

Multiplying eqⁿ ① and ② , ② and ③ and ③ and ① and adding together and simplifying , we will get .

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$


$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$
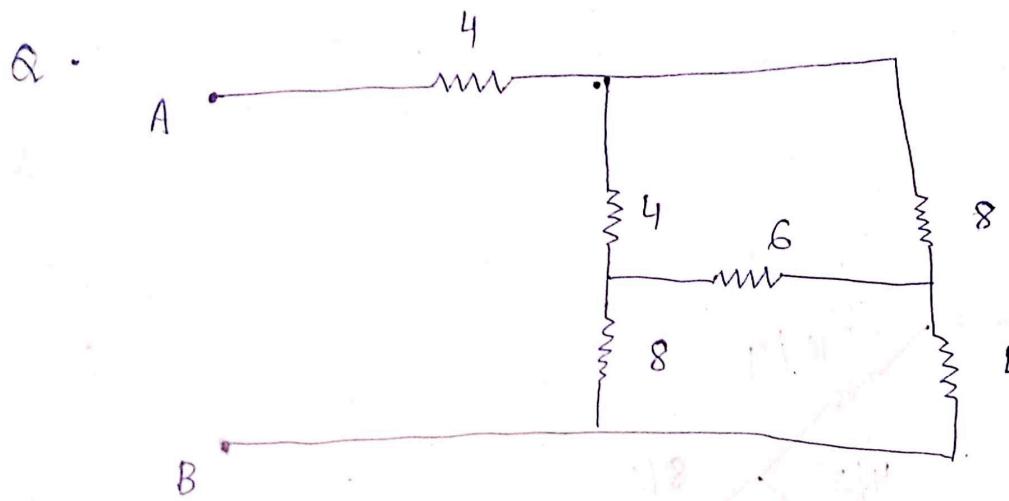
$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$



find R_{AB} ?

sol'

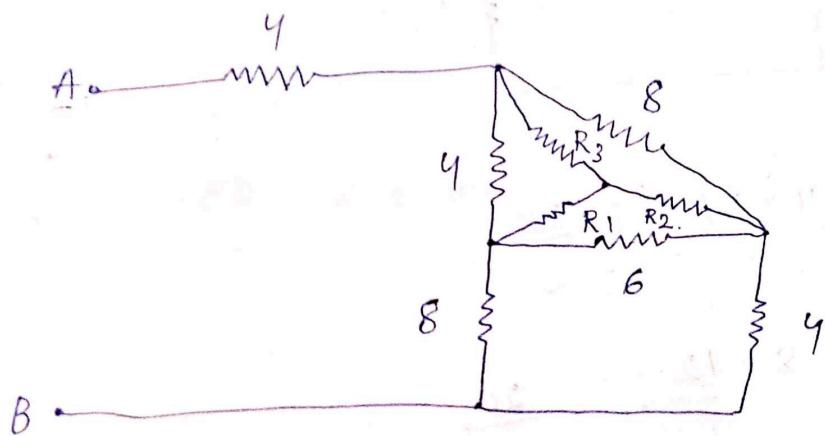

$$R_1 = \frac{4 \times 6}{4 + 6 + 8} = \frac{24}{18} = \frac{4}{3}$$

$$R_2 = \frac{8 \times 6}{4 + 6 + 8}$$


$$= \frac{48}{18}$$

$$= \frac{8}{3}$$

$$R_3 = \frac{4 \times 8}{4 + 6 + 8}$$

$$= \frac{32}{18}$$


$$= \frac{16}{9}$$

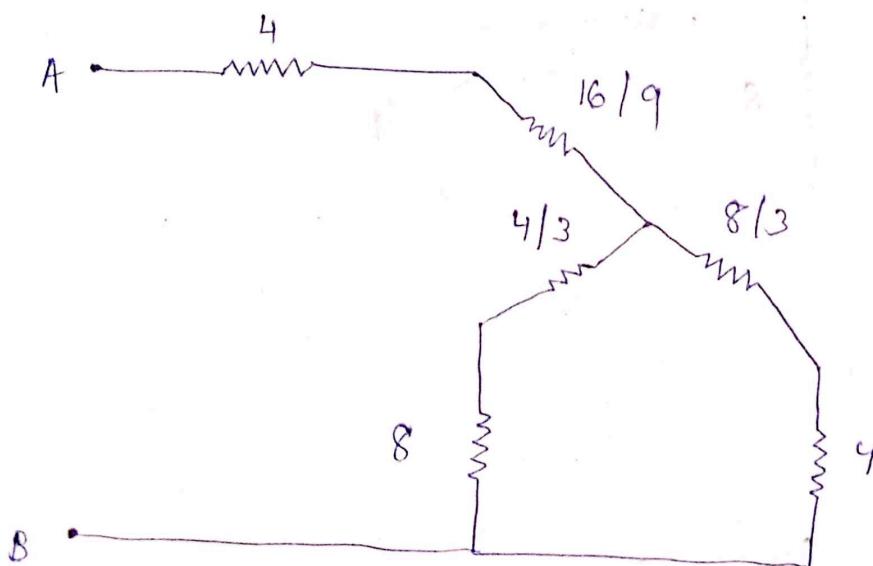

$$\frac{4}{3} + 8 = \frac{4 + 24}{3} = \frac{28}{3}$$

$$\frac{8}{3} + 4 = \frac{8 + 12}{3} = \frac{20}{3}$$
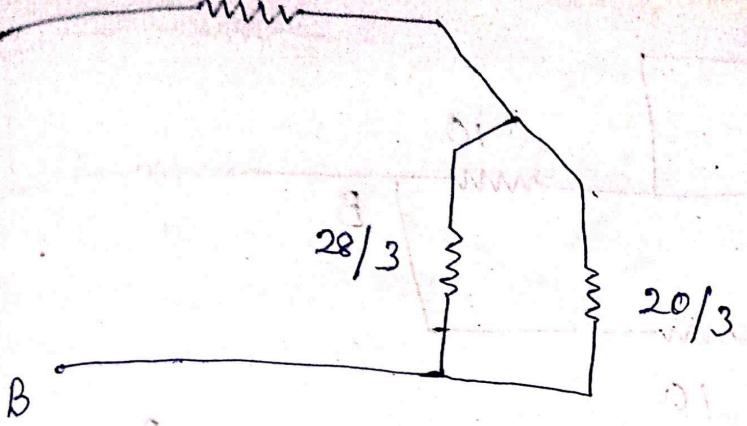
$$4 + \frac{16}{9} = \frac{36 + 16}{9} = \frac{52}{9}$$




$$\frac{28}{3} \parallel \frac{20}{3} = \frac{\frac{28}{3} \times \frac{20}{3}}{\frac{28}{3} + \frac{20}{3}}$$

$$\begin{array}{r} 560 \\ \hline 9 \\ \hline 48 \\ \hline 3 \end{array}$$

$$= \frac{560}{3 \times 48}$$

$$= 3.8$$


$$52/9$$

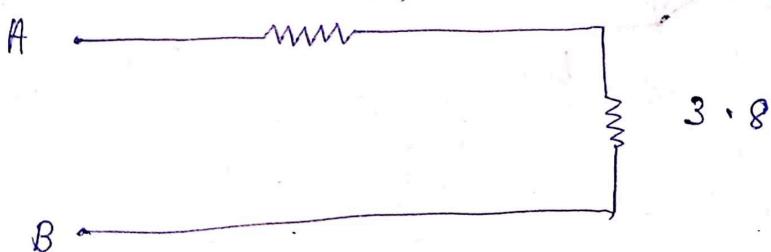

$$R_{AB} = \frac{52}{9} + 3.8$$



$$= 5.7 + 3.8$$

$$= 9.5 \Omega$$

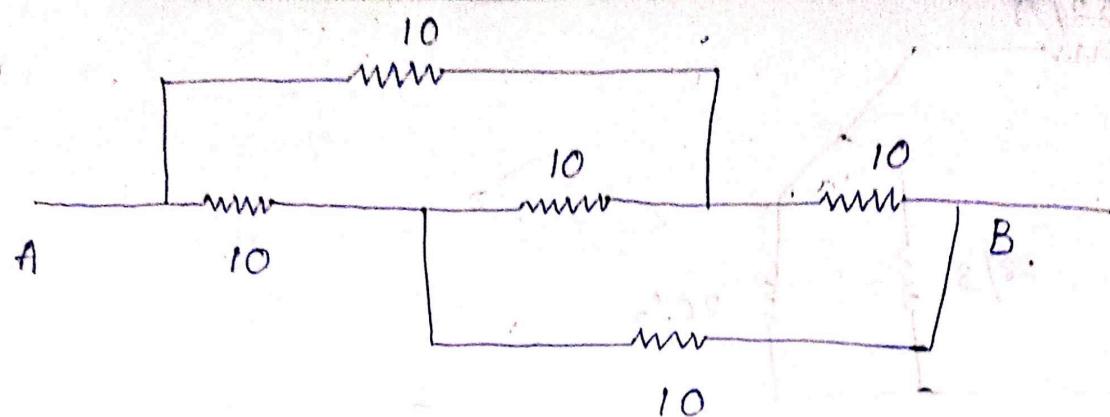

Find the equivalent resistance bet' the terminal A and B.

sod?

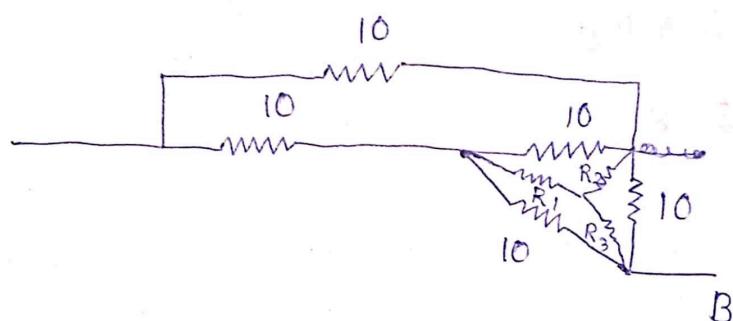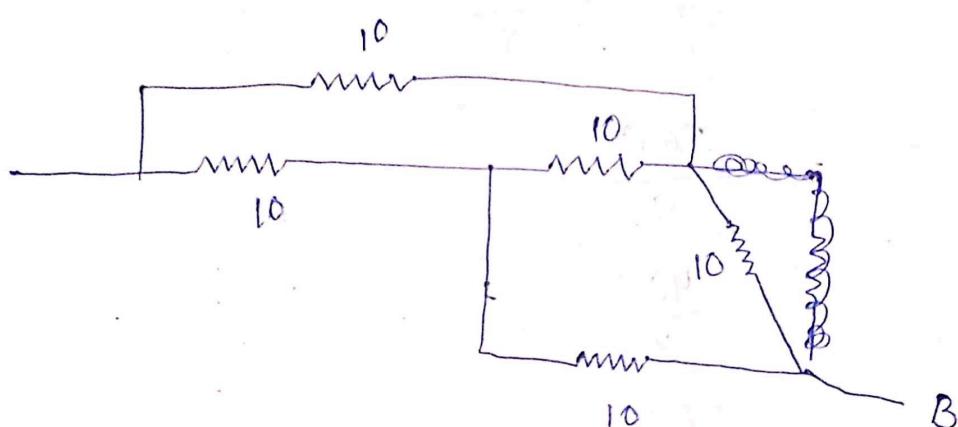


$$R_1 = \frac{10 \times 10}{10 + 10 + 10}$$


$$\frac{100}{30}$$

$$= \frac{10}{3}$$

$$R_1 = R_2 = R_3 = \frac{10}{3}$$

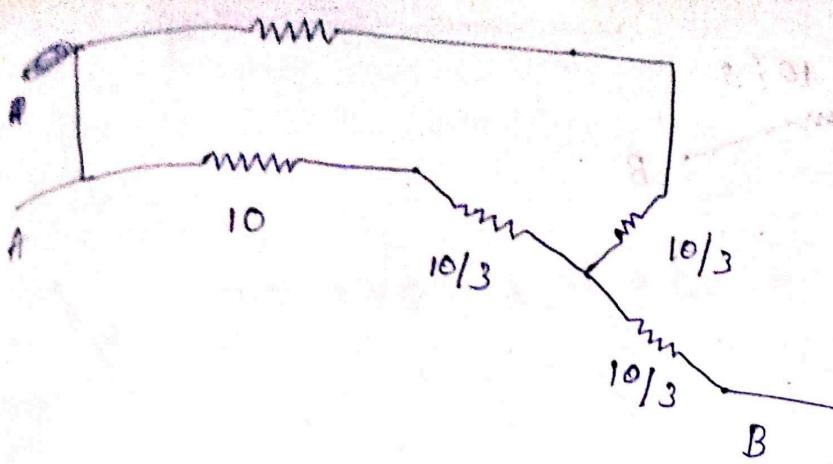
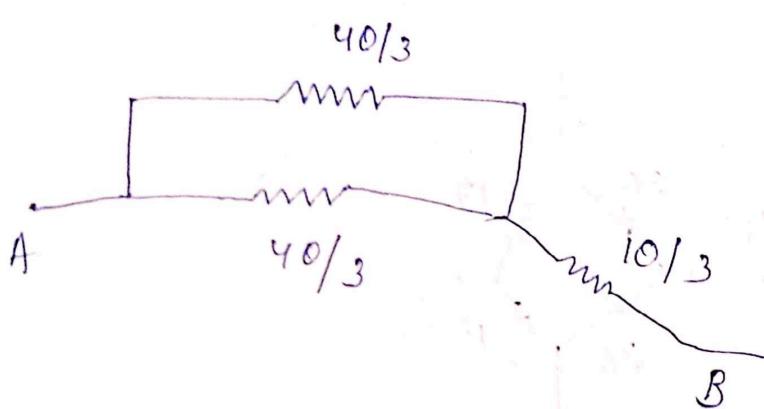
$$10 + \frac{10}{3} = \frac{30 + 10}{3} = \frac{40}{3}$$




$$\begin{aligned} & \frac{40}{3} \parallel \frac{40}{3} \\ & = \frac{40}{3} \times \frac{40}{3} \\ & \quad \underline{\underline{\qquad}} \\ & \quad \frac{40}{3} + \frac{40}{3} \end{aligned}$$


$$= \frac{\frac{1600}{9}}{\frac{80}{3}}$$

$$= \frac{1600}{9} \times \frac{3}{80}$$

$$= \frac{20}{3}$$

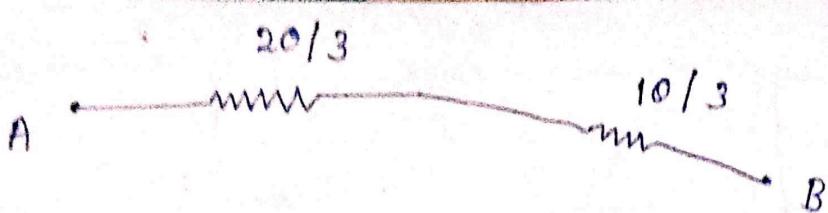


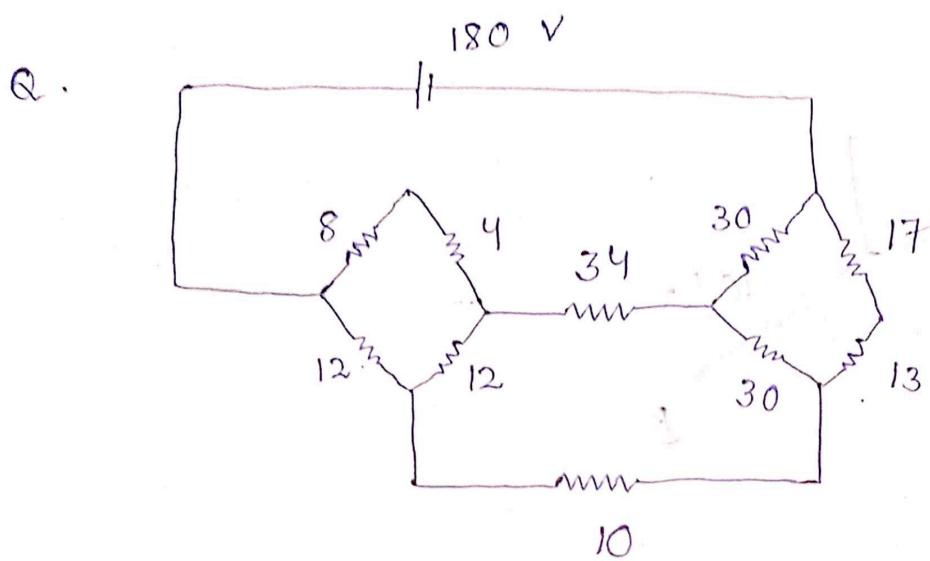
$$\begin{aligned}
 R_{AB} &= \frac{20}{3} + \frac{10}{3} \\
 &= \frac{30}{3} \\
 &= 10 \Omega \quad (\text{Ans})
 \end{aligned}$$



calculate the current through 10Ω resistor.

Sol'

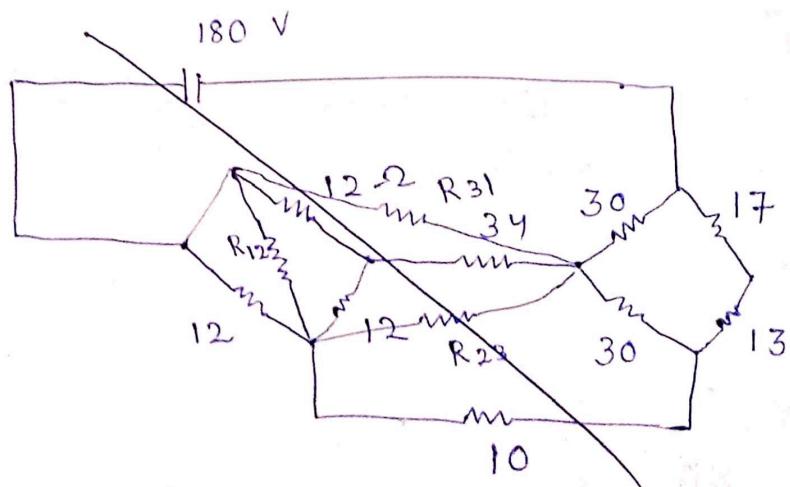

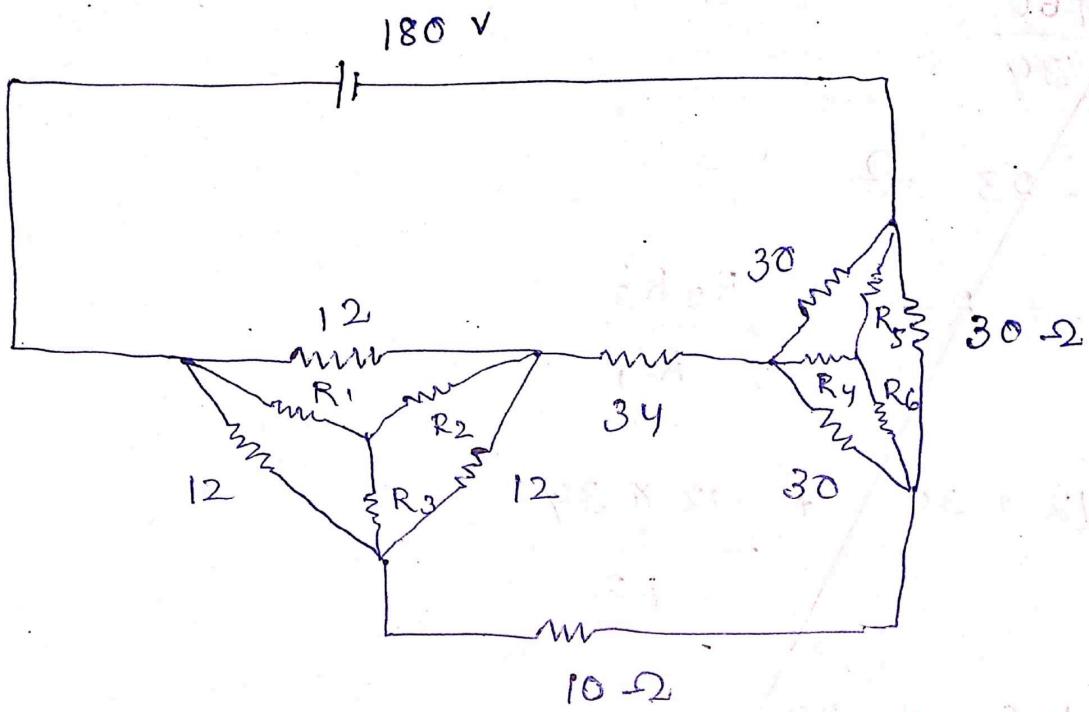




$$R_1 = \frac{12 \times 12}{12 + 12 + 12}$$

$$= \frac{144}{36}$$

$$= 4 \Omega = R_2 = R_3$$

$$R_4 = \frac{30 \times 30}{30 \times 30 + 30}$$
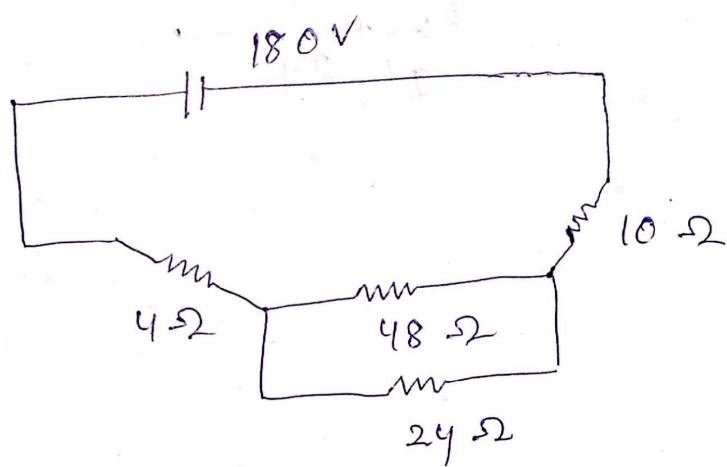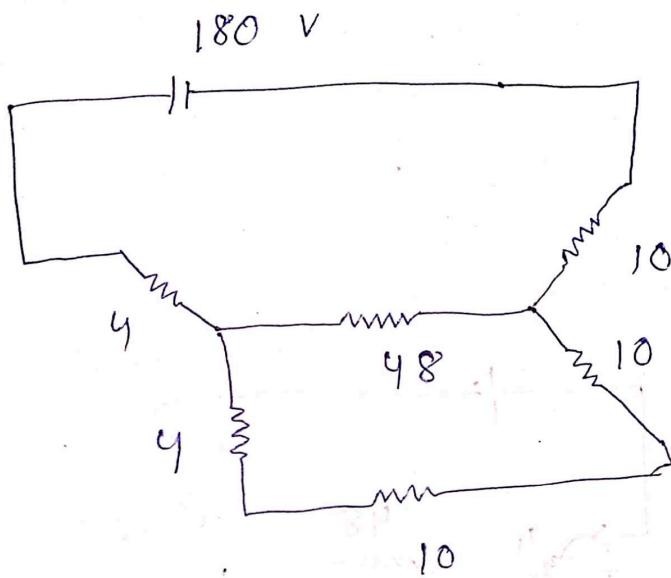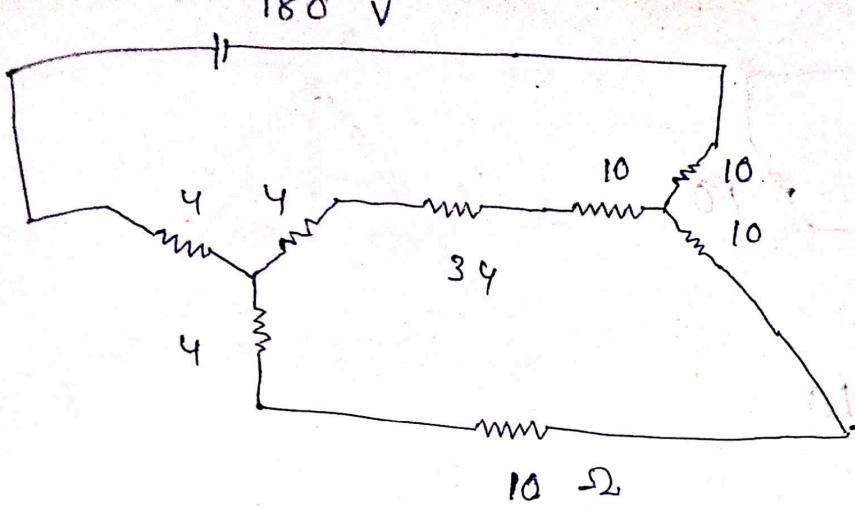
$$= \frac{900}{90} = 10 \Omega = R_5 = R_6$$



$$48 \parallel 24 = \frac{48 \times 24}{48 + 24}$$

$$= \frac{1152}{72}$$

$$= 16$$